

Figure P12.6

7 The linear time-invariant circuit of Fig. P12.7a, having a digraph shown in Fig. P12.7b, is in the sinusoidal steady state. From the digraph a tree is picked as shown in Fig. P12.7c.

(a) Write the fundamental cut-set matrix \mathbf{Q} .

(b) Calculate the cut-set admittance matrix \mathbf{Y}_q .

(c) Write the cut-set equations in the frequency domain in terms of the cut-set voltage and the current source:

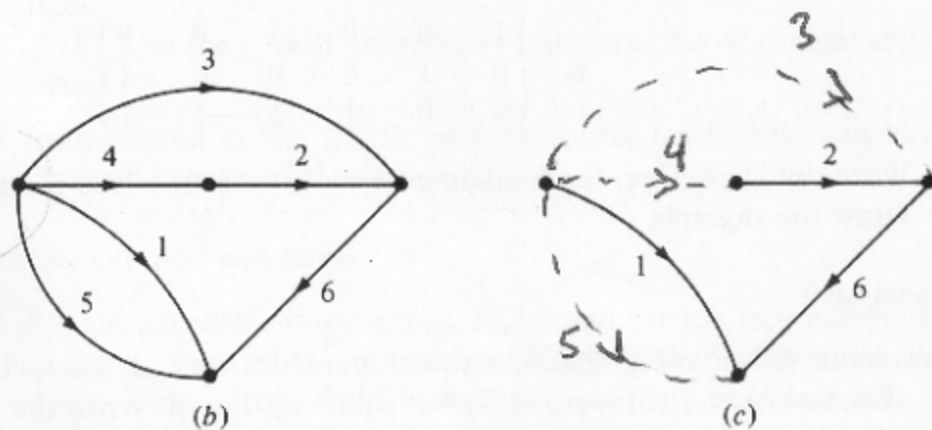
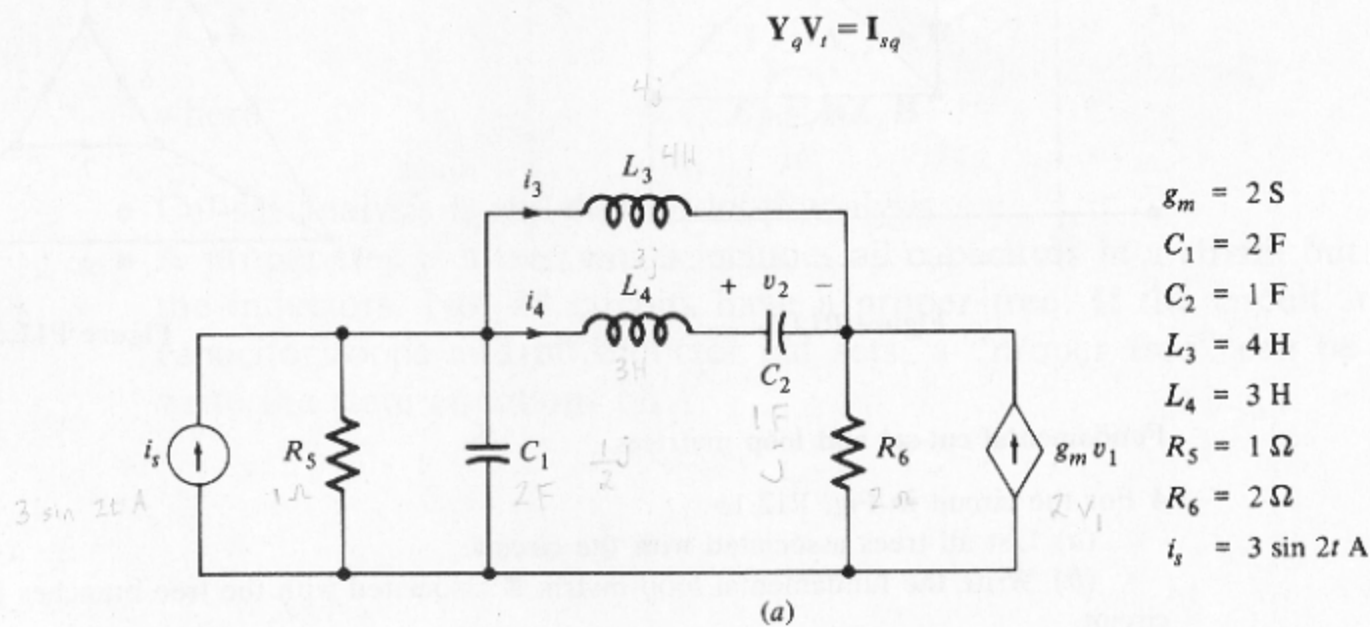


Figure P12.7