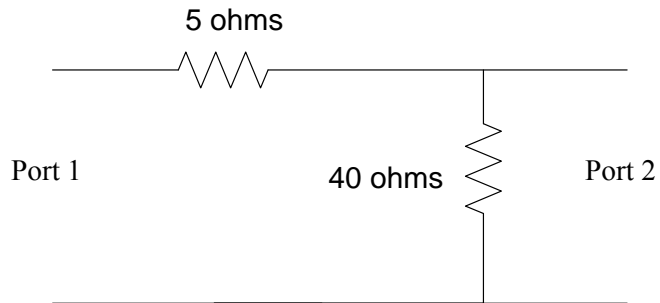



ELC 4383 – RF/Microwave Circuits I
Chapter 4 Supplemental Homework

S4.1. Consider the two-port network given below:



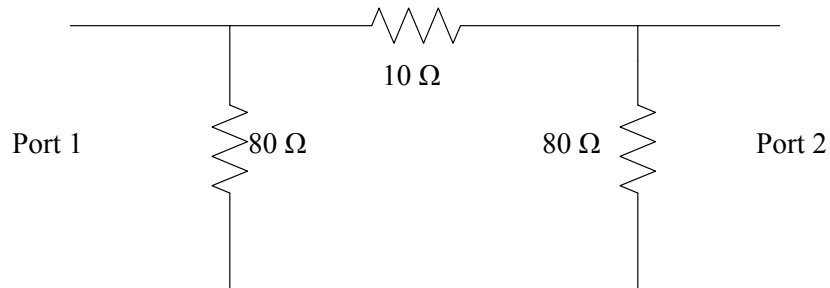
- (a) Find S_{11} for $Z_0 = 50 \Omega$.
- (b) Find S_{21} for $Z_0 = 50 \Omega$.

S4.2. Consider the two-port network given below:



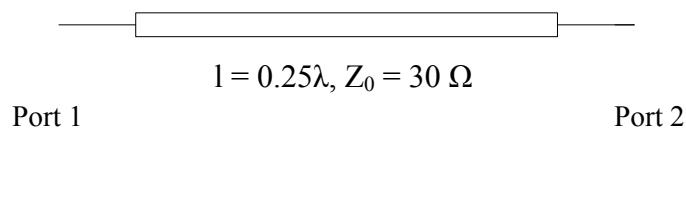- (a) Find S_{11} for $Z_0 = 50 \Omega$.
- (b) Find S_{21} for $Z_0 = 50 \Omega$.

S4.3. Consider the following two-port network:



- (a) Find S_{11} , referenced to $Z_0 = 50 \Omega$.
- (b) Find S_{21} , referenced to $Z_0 = 50 \Omega$.

S4.4. Consider a two-port network with S-parameters (taken with respect to $Z_0 = 50 \Omega$) given as follows:

$$[S] = \begin{bmatrix} 0.3 \angle 0^\circ & 0.6 \angle 50^\circ \\ 0.6 \angle 50^\circ & 0.3 \angle 0^\circ \end{bmatrix}$$


- Is the network reciprocal? Why or why not?
- Is the network lossless? Show that your answer is correct based on the mathematical equation identities regarding S-parameters for lossless networks.
- What is the input reflection coefficient looking into port 1 if a 100Ω resistor is connected as the load to port 2?

S4.5. Consider a two-port network with S-parameters (taken with respect to $Z_0 = 50 \Omega$) given as follows:

$$[S] = \begin{bmatrix} 0.2 \angle 90^\circ & 0.2 \angle 0^\circ \\ 0.9 \angle 100^\circ & 0.2 \angle -90^\circ \end{bmatrix}$$

- Is the network reciprocal? Why or why not?
- Is the network lossless? Show that your answer is correct based on the mathematical equation identities regarding S-parameters for lossless networks.
- What is the input reflection coefficient looking into port 1 if a 20Ω resistor is connected as the load to port 2?

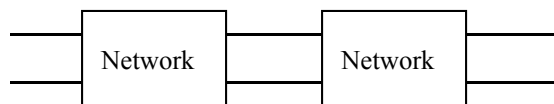S4.6. Consider a problem in which two two-port networks, each possessing the given S-parameters, are placed in cascade:



The S-Parameters for each individual network (with $Z_0 = 50 \Omega$) are:

$$S_{11} = 0.1$$

$$S_{12} = 0.9$$

$$S_{21} = 0.9$$

$$S_{22} = 0.1$$

Find the ABCD matrix for the cascade combination of the networks.