

ELC 4383 – RF/Microwave Circuits I

Chapter 7 Supplemental Homework

S7.1. A 2 W power source is connected to the input of a directional coupler with $C = 10$ dB, $D = 30$ dB, and an insertion loss of 1 dB. Find the output powers (in dBm) at the through, coupled, and isolated ports. Assume all ports to be matched.

S7.2. A 5 W power source is connected to the input of a directional coupler with $C = 5$ dB, $I = 25$ dB, and an insertion loss of 2 dB.

(a) Find the output powers (in dBm) at the through, coupled, and isolated ports. Assume all ports to be matched.

(b) Find the directivity, D , in dB.

S7.3. Design a single-section microstrip coupled-line coupler with a coupling of 12 dB and a system impedance of 50Ω . If the coupler is to be made in microstrip with $\epsilon_r = 10$ and d (substrate thickness) = 1.8 mm, use Figure 7.30 on page 350 of your text to find the necessary width of the lines and separation between the lines.

S7.4. Design a single-section microstrip coupled-line coupler with a coupling of 8 dB and a system impedance of 50Ω . If the coupler is to be made in microstrip with $\epsilon_r = 10$ and d (substrate thickness) = 1.5 mm, use Figure 7.30 on page 350 of your text to find the necessary width of the lines and separation between the lines.