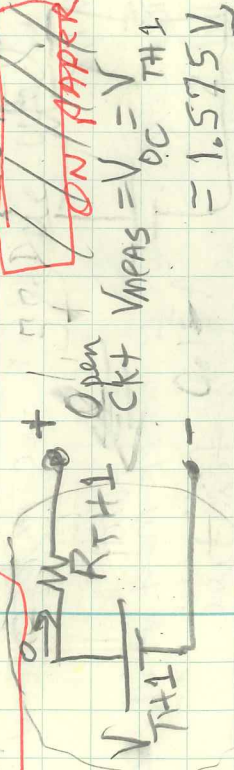


Theremin Eq. of 8 D batteries in series



HW #1. Due Wed (on paper)

Put 8 of the batteries shown here in series.


Solve for Thv Eq. of

8 identical batteries in series

$$V_{OC} (NO \text{ CURRENT}) = 8 \times 1.575 \text{ V}$$

Turn off the sources (i.e. $V=0$)

$$R_{TH} = 8 \times (0.328)$$

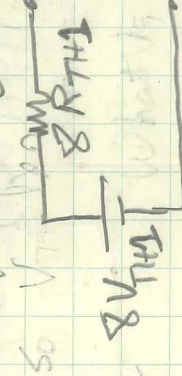

Open ckt voltage increases by 8. $\rightarrow$ Can produce 8 times the S.C. current is same as 1 batt

Find the Load that will consume 10 WATTS

Theremin's Theorem says that an two nodes of a linear circuit can be represented by one voltage source and one resistor



0 for open ckt

$$KVL, -V_{TH} + I R_{TH} + V_{OUT} = 0$$

$$SO V_{TH} = V_{OUT \text{ OPEN CKT}}$$


Then short it, Measure I_{SC}



$$SO -V_{TH} + I_{SC} R_{TH} = 0$$

$$R_{TH} = V_{TH} / I_{SC}$$

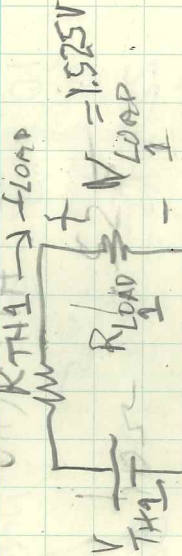Shorting can cause damage, so connect a Resistor to the output that will have a reasonable current, and test under load instead of short ckt (50



$$KVL, -V_{TH1} + I_{LOAD} R_{TH1} + I_{LOAD} R_{LOAD} = 0$$

$$R_{TH1} = 10 \Omega$$

$$SO I_{LOAD} = \frac{V_{LOAD}}{R_{LOAD}} = \frac{1.575}{10} = 0.1575 \text{ A}$$

$$SO R_{TH1} = \frac{1.575 - 1.575}{0.1575} = 0.328 \Omega$$

$$R_{TH1} = 0.328 \Omega$$

In this case we know

$$R_{LOAD1} = 10 \Omega$$

$$SO I_{LOAD1} = \frac{V_{LOAD}}{R_{LOAD}} = \frac{1.575}{10} = 0.1575 \text{ A}$$

$$SO R_{TH1} = \frac{1.575 - 1.575}{0.1575} = 0.328 \Omega$$

$$R_{TH1} = 0.328 \Omega$$

Open ckt voltage increases by 8. $\rightarrow$ Can produce 8 times the S.C. current is same as 1 batt

Find the Load that will consume 10 WATTS

Theremin's Theorem says that an two nodes of a linear circuit can be represented by one voltage source and one resistor



0 for open ckt

$$KVL, -V_{TH} + I R_{TH} + V_{OUT} = 0$$

$$SO V_{TH} = V_{OUT \text{ OPEN CKT}}$$

Then short it, Measure I_{SC}



$$SO -V_{TH} + I_{SC} R_{TH} = 0$$

$$R_{TH} = V_{TH} / I_{SC}$$

Shorting can cause damage, so connect a Resistor to the output that will have a reasonable current, and test under load instead of short ckt (50

Our Case


$$V_{TH} = 1.575 \text{ Volts} \quad R_{TH} = 10 \Omega \quad V_{LOAD} = 1.525 \text{ V} \quad I_{LOAD} = 0.15 \text{ A}$$

Matches the measured current 0.15 A

Now, use KVL, $-V_{TH} + IR_{TH} + V_{LOAD} = 0$, $R_{TH} = \frac{V_{TH} - V_{LOAD}}{0.15 \text{ A}}$

$$R_{TH} = \frac{1.575 - 1.525 \text{ Volts}}{0.15 \text{ A}} = \frac{0.05 \text{ Volts}}{0.15 \text{ A}} = \frac{1}{3} \Omega$$

Battery Thev Eg.

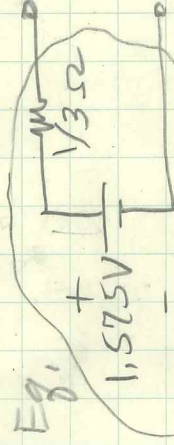

Class D $V_{OC} = 1.575 \text{ V}$, $I = \frac{1.533}{10} = 0.1533 \text{ A}$, $R_{TH} = \frac{1.575 - 1.533}{0.1533} = 0.274 \Omega$

C $V_{OC} = 1.605 \text{ V}$, $I = \frac{1.543}{10} = 0.1543 \text{ A}$, $R_{TH} = 0.402 \Omega$

AA $V_{OC} = 1.620 \text{ V}$, $I = \frac{1.564}{10} = 0.1564 \text{ A}$, $R_{TH} = 0.358 \Omega$


AAA $V_{OC} = 1.620 \text{ V}$, $I = \frac{1.555}{10} = 0.1555 \text{ A}$, $R_{TH} = 0.418 \Omega$

9V $V_{OC} = 9.61 \text{ V}$, $I = \frac{6.5}{10} = 0.65 \text{ A}$, $R_{TH} = 4.18 \Omega$

$$V_{TH} = 9.61 \text{ V} + \frac{R_{TH}}{10 \Omega} \cdot 0.65 \text{ A} = 9.61 - 6.50 = 4.18 \Omega$$

HW #6 How to handle multiple batteries

HW #2 Friday

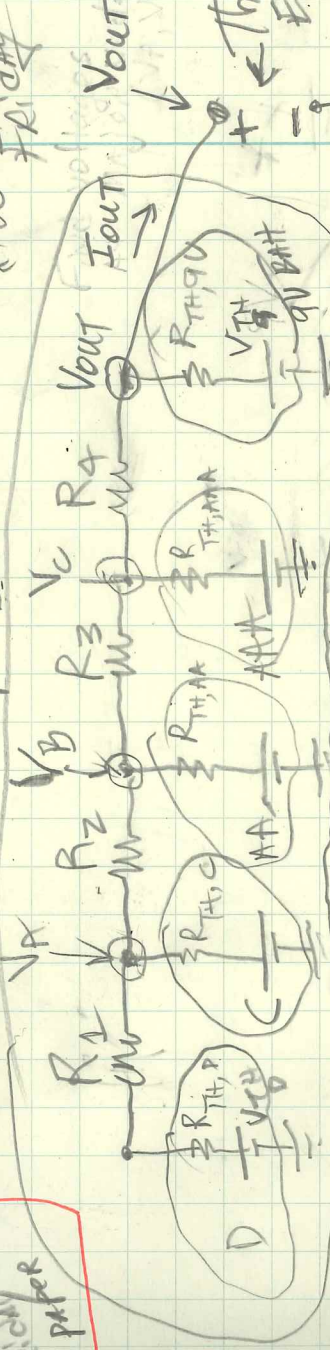

Use Thev. Case 1 (ie, turn off voltage sources) and develop an expression (variables only) to determine R_{TH} for the combined circuit.

Work from left to right to get the expression for R_{TH} at the output.

Use the battery R_{TH} values, and $R_1 = 15$, $R_2 = 22$, $R_3 = 33$, $R_4 = 48 \Omega$ to solve for R_{TH} at the output.

Use the Nodal method to form the matrix needed to solve for V_A , V_B , V_C , V_{OUT} . NO NUMBERS.

Same ground as inside the circuit.