


HW #1, cont.

Power is $I^2 R$ and VI . V and I are linear, but their product (Power) is non linear.

I.E., double the voltage across a resistor, and the power increases by a factor of 4. Nevertheless, we can attempt to find the R_{LOAD} that will consume 10 W.

Stick with the equations!

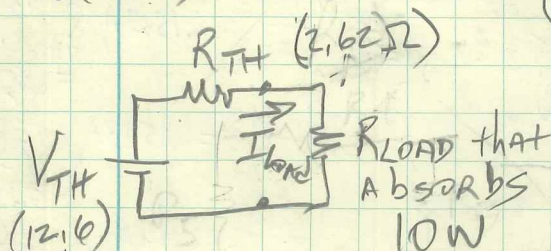$8V_{TH}$ $\frac{8R_{TH}}{W}$ $\rightarrow I_L$ $+ V_L$ $-$ R_{LOAD} $\rightarrow$ What R_{LOAD} results in $P_L = 10 W$?
 $8(0.328) = 2.62 \Omega$
 $8(1.575) = 12.6 V$
 $V_{LOAD} I_{LOAD} = 10 W$, $\frac{V_{LOAD}^2}{R_{LOAD}} = 10 W$, $I_{LOAD}^2 R_{LOAD} = 10 W$
 One Equation shown three ways



CAN this battery do it? What is its MAX power load?

$$P_{LOAD} = V_{LOAD} I_{LOAD} = (V_{TH} - I_{LOAD} R_{TH}) (I_{LOAD})$$

$$P_{LOAD} = V_{TH} I_{LOAD} - R_{TH} I_{LOAD}^2$$

Power out of $\frac{V}{I}$
 Power consumed by R_{TH}
 Power consumed by $R_{LOAD} = P_{LOAD}$

Find the I_{LOAD} that results in MAX P_{LOAD}

$$\frac{\partial P_{LOAD}}{\partial I_{LOAD}} = V_{TH} - 2R_{TH} I_{LOAD} = 0$$

so for


$$\frac{V_{TH}}{2}$$

MAX P_{LOAD} ,

$$I_{LOAD} = \frac{V_{TH}}{2R_{TH}}$$

so $[R_{TH} + R_{TH}]$ yields MAX LOAD POWER

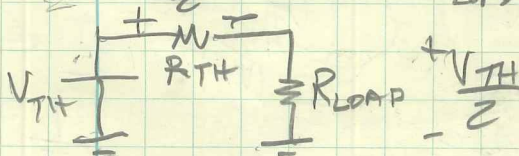so $R_{LOAD} = R_{TH}$ yields MAX P_{LOAD}



For MAX load power, Internal Losses equals load power, 50% Efficient (bad)
 Load voltage is $\frac{1}{2} V_{TH}$ (bad)

Our case, $P_{MAX LOAD} = \left[\frac{1}{2} V_{TH} \right] \left[\frac{V_{TH}}{2R_{TH}} \right] = \frac{V_{TH}^2}{4R_{TH}} = \frac{(12.6)^2}{4(2.62)} = 15.15 W$

LOAD VOLTAGE $\times$ LOAD CURRENT

HW #1, CONT.

SO, 10W output is possible.

Refer back to

$$P_{LOAD} = (V_{TH} - I_{LOAD} R_{TH}) (I_{LOAD})$$

$$P_{LOAD} = V_{TH} I_{LOAD} - R_{TH} (I_{LOAD})^2, \text{ so}$$

$$P_{LOAD} - V_{TH} I_{LOAD} + R_{TH} (I_{LOAD})^2 = 0$$

$$(I_{LOAD})^2 - \frac{V_{TH}}{R_{TH}} (I_{LOAD}) + \frac{P_{LOAD}}{R_{TH}} = 0 \quad \text{QUADRATIC}$$

$$I_{LOAD} = \frac{\frac{V_{TH}}{R_{TH}} \pm \sqrt{\left(\frac{V_{TH}}{R_{TH}}\right)^2 - 4 \frac{P_{LOAD}}{R_{TH}}}}{2}$$

Two possible values

$$I_{LOAD} = \frac{1}{2} \left[4.81 \pm \sqrt{(4.81)^2 - 4 \left(\frac{10}{2.62} \right)} \right]$$

$$= \frac{1}{2} \left[4.81 \pm \sqrt{23.1 - 15.27} \right] = \frac{4.81 \pm 2.79}{2}$$

= 3.8A AND 1.01Amps both work but!

High Amps,
Low EFF.Low Amps
Higher EFF

INEFFICIENT

For the 3.8A case, $V_{LOAD} = 12.6 - (3.8)(2.62) = 2.64V$

$$R_{LOAD} = \frac{2.64V}{3.8A} = 0.697 \Omega$$

$$P_{LOAD} = \frac{(2.64V)^2}{0.697 \Omega} = 10.0W!$$

EFFICIENT

For the 1.01A case

$$V_{LOAD} = 12.6 - (1.01)(2.62) = 9.95V$$

$$R_{LOAD} = \frac{9.95V}{1.01A} = 9.85 \Omega$$

$$P_{LOAD} = \frac{(9.95)^2}{9.85} = 10.1W!$$

