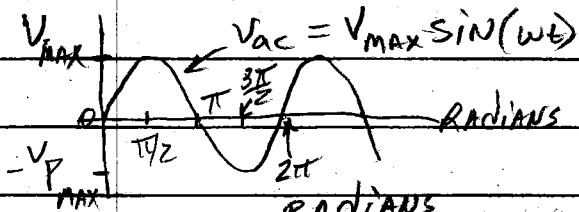


2021-0927a

C properties,

$$i_c(t) = C \frac{dv(t)}{dt}$$

We'll use $i = C \frac{dv}{dt}$
[NO "t"]



$$\omega = \frac{\text{RADIAN}}{\text{SEC}}$$

$$360^\circ = 2\pi \text{ RADIAN}$$

$$\begin{aligned} \leftarrow \text{1 cycle} \rightarrow \\ = 360^\circ \\ = 2\pi \text{ RADIAN} \end{aligned}$$

$$1 \text{ Hz} = 2\pi \frac{\text{RAD}}{\text{SEC}}$$

$$= 1 \text{ cycle/sec}$$

$$60 \text{ Hz} = 60 \text{ cycles/sec} = 60 \times 60 \frac{\text{Rev}}{\text{SEC}}$$

$$\pi/2 = 90^\circ$$

$$\begin{aligned} \pi &= 180^\circ \\ \pi/2 &= 90^\circ \end{aligned}$$

So, power grid is equivalent to 3600 $\frac{\text{rpm}}{\text{rpm}}$ = 3600 rpm


Actual generators usually operate at 1800 rpm with double set of windings to make each revolution produce two cycles

Wind farms about $\rightarrow$ one revolution per 3 sec. max.

Gear ratio and variable excitation convert it to 60 Hz.

Tip speed for max power is about 6 times wind speed.

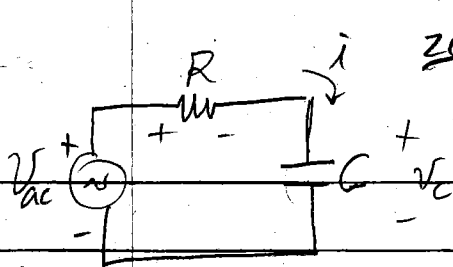Capacitors, $i = C \frac{dv}{dt}$ is linear because in steady state because the i of A freq. will produce only the same freq. of v , and vice versa. Excite it with F Hz, response is only F Hz (in steady state)



2021-0927b

$$\text{KVL, } -V_{ac} + Ri + V_c = 0$$

$$i = C \frac{dV_c}{dt}$$

$$\text{So } -V_{ac} + R \left(C \frac{dV_c}{dt} \right) + V_c = 0$$

$$-\frac{V_{ac}}{RC} + \frac{dV_c}{dt} + \frac{V_c}{RC} = 0$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = 0 + \frac{V_{ac}}{RC}$$

Known

Start with a simple case R

where $V_{ac} = 0$,

$$\left[\begin{array}{c} \text{switch} \\ t=0 \end{array} \right] C = A \text{ volts}$$

Close switch at $t=0^+$

$$\frac{dV_c}{dt} = -\frac{V_c}{RC}$$

Hmmm!, try $V_c = Ae^{-\alpha t} + B$

$$\frac{dV_c}{dt} = -\alpha Ae^{-\alpha t}$$

$$-\alpha Ae^{-\alpha t} = -\frac{1}{RC} [Ae^{-\alpha t} + B] = \frac{-A}{RC} e^{-\alpha t} - \frac{B}{RC}$$

$$-\alpha Ae^{-\alpha t} = \frac{-A}{RC} e^{-\alpha t} - \frac{B}{RC}$$

So, if $\alpha = \frac{1}{RC}$ & $B=0$, $V_c = Ae^{-t/RC}$

$$V_c(0) = Ae^0 = A, \text{ so } V_c = V_c(0) e^{-t/RC}$$


NATURAL decay exponential, τ is "time constant"


$$\text{Define } \tau = \frac{1}{\alpha}, \text{ so } \tau = RC \text{ seconds}$$

$$t=0 \quad t \quad t=\tau \quad e^{-\frac{\tau}{\tau}} = e^{-1}$$

$$t=2\tau \quad e^{-2} =$$

$$t=3\tau \quad e^{-3} =$$

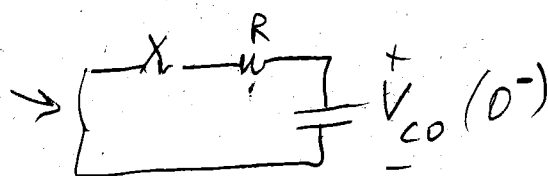2021-09-29a
Now, instead of $\rightarrow$ 

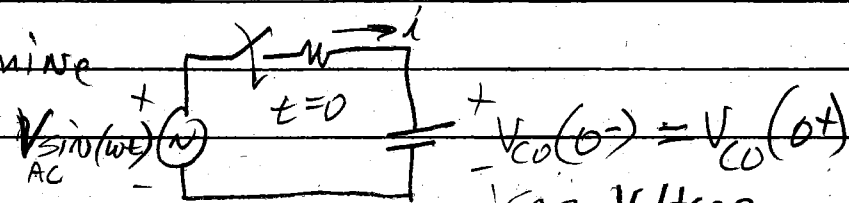We examine 

$$-V_{ac} + Ri + V_c = 0$$

$$i = C \frac{dV_c}{dt}, i = \frac{V_{ac} - V_c}{R}$$

combine

Cap. Voltage
CANNOT CHANGE
INSTANTLY

(KVL) $C \frac{dV_c}{dt} = \frac{V_{ac} - V_c}{R}$, $\frac{dV_c}{dt} + \frac{V_c}{RC} - \frac{V_{ac}}{RC} = 0$ Known

We can still expect there to be a component of V_c like $[Ae^{-t/\tau} + B]$ (not same A, B as before)

And a component due to $V_F \sin(\omega t)$

There is only one equation that works, and if we find an equation that works, it is the solution. It will likely be necessary to add a phase shift in the sine wave. $V_F \sin(\omega t + \theta)$.

$$\frac{d}{dt} [Ae^{-t/\tau} + B + V_F \sin(\omega t + \theta)] + \frac{1}{RC} [Ae^{-t/\tau} + B + V_F \sin(\omega t + \theta)] - \frac{V_{ac} \sin(\omega t)}{RC} = 0$$

V_c

2021-0929(6)

$$\left[-\frac{t}{\tau} A e^{-t/\tau} + \omega V_F \cos(\omega t + \theta) \right]$$

$$+ \left[\frac{A}{RC} e^{-t/\tau} + \frac{B}{RC} + \frac{V_F}{RC} \sin(\omega t + \theta) \right]$$

$$- \frac{V_{AC}}{RC} \sin(\omega t) = 0$$

goes to zero

Collect Terms

must be zero


$$e^{-t/\tau} \left[-\frac{t}{\tau} + \frac{A}{RC} \right] + \frac{B}{RC} + V_F \left[\omega \cos(\omega t + \theta) + \sin(\omega t + \theta) \right] = 0$$

$$\text{When } t=0, \left[-\frac{0}{\tau} + \frac{A}{RC} \right] + \frac{B}{RC} + V_F [\omega \cos(\theta) + \sin(\theta)] = 0$$

$$\text{So } A=0 \Rightarrow \frac{B}{RC} + V_F [\omega \cos(\theta) + \sin(\theta)] = 0$$

When t is large, $e^{-t/\tau} \rightarrow 0$, then
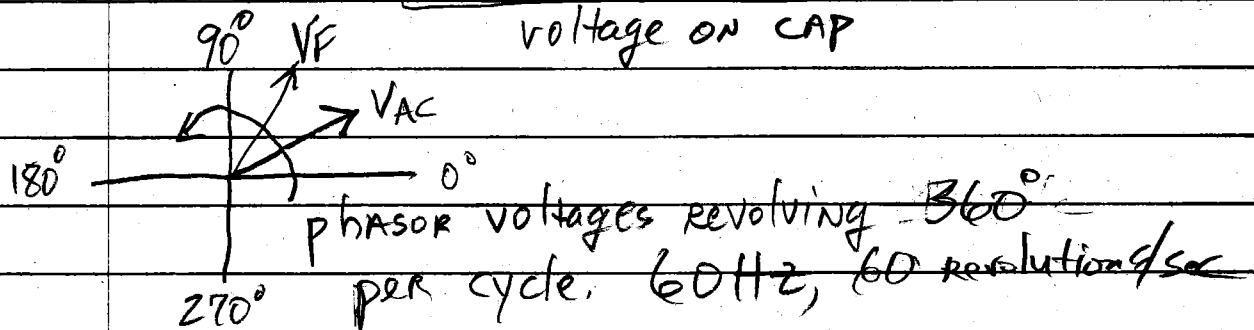
$$\text{So } \frac{B}{RC} + V_F [\omega \cos(\omega t + \theta) + \sin(\omega t + \theta)] = 0$$



Steinmetz - the genius who developed the concept of PHASOR ANALYSIS FOR S.S. A.C.