
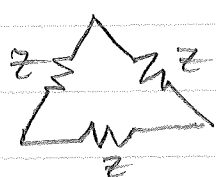


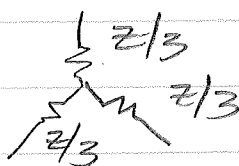2.42 wye-equivalent
Draw the one-line diagram



equiv.




$$\frac{12+j9}{3} = 4+j3$$

$$208V_{LL} \div \sqrt{3} = 120V_{LN}$$

$\frac{\text{RMS Line-to-Line}}{\text{RMS Line-to-Neutral}}$

One line (phase A)

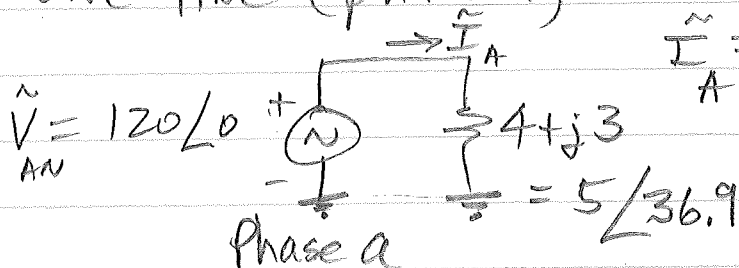


$$\tilde{I}_A = \frac{120\angle 0}{5\angle 36.9} = 24\angle -36.9^\circ \text{ A RMS}$$


$$S_A = \tilde{V}_{AN} \tilde{I}_A^* = (120\angle 0)(24\angle -36.9)^\star = (120\angle 0)(24\angle +36.9)$$

$$= 2880\angle 36.9 \text{ VA} = \underset{\text{W}}{2303} + j\underset{\text{VAR}}{1729}$$

Power Triangle

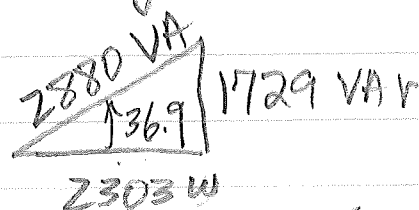

$\tilde{V}_{AN}, \tilde{I}_A$ phasors

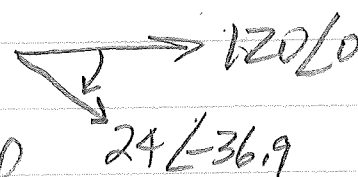


Angles negated


Load receives
P and positive Q

lagging $\tilde{I}$

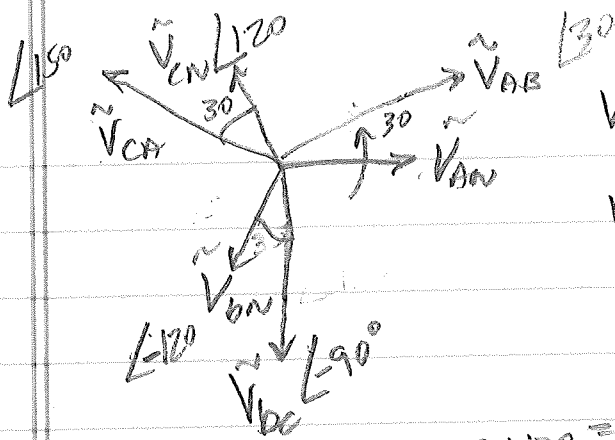Phases b & c have same P, Q. $\tilde{V}_{bN}, \tilde{I}_b$ lag by 120°
 $\tilde{V}_{cN}, \tilde{I}_c$ lead by 120°



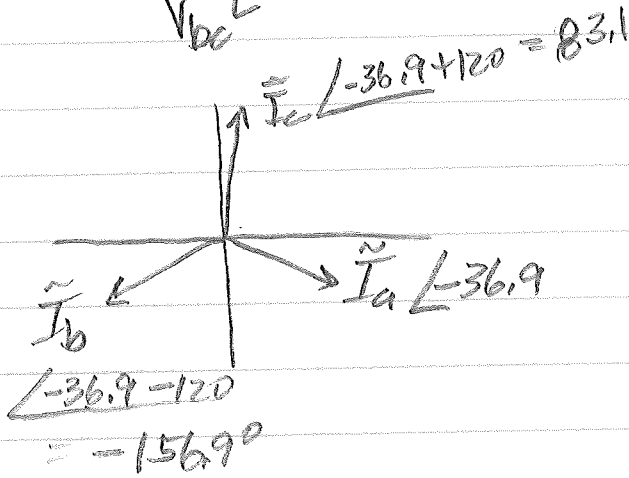V_{L-L} leads $L-N$ by 30°
 V_{LL} is $\sqrt{3}$ larger




$\hat{I}_{ab}$ leads I_a by 30° ,
 And is $\sqrt{3}$ smaller

$$\hat{I}_{ab} = \frac{24}{\sqrt{3}} \angle -36.9 + 30^\circ$$

$$\hat{I}_{bc} = \frac{24}{\sqrt{3}} \angle -156.9 + 30^\circ$$

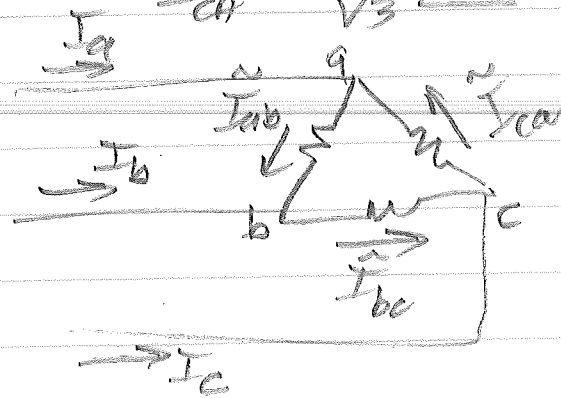
$$\hat{I}_{ca} = \frac{24}{\sqrt{3}} \angle 83.1 + 30^\circ$$



If you want V_{AB} to be $\angle 0$, then
 take away 30° from every $V \neq I$
 Angle

3/7

2.44 Draw one-line diagram

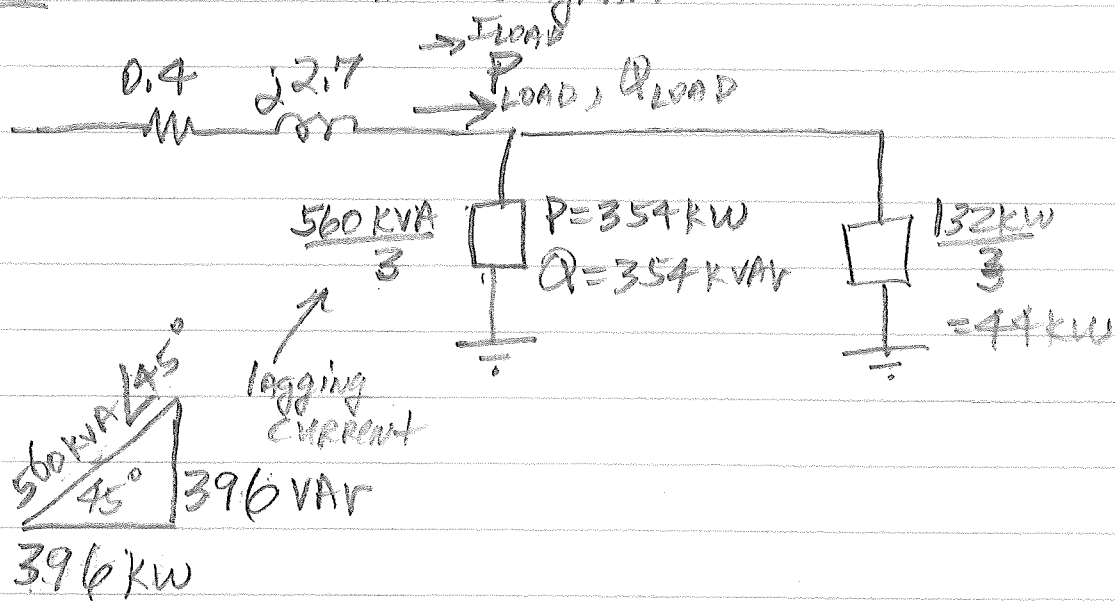

LN Voltage at load is $\frac{2200\sqrt{3}}{\sqrt{3}} = 2200 \text{ V}_{rms}$

Conservation of power

$$\left. \begin{aligned} P_{LOAD} &= (396 + 132) = 528 \text{ kW} \\ Q_{LOAD} &= (354 + 0) = 354 \text{ kVAR} \end{aligned} \right\} \begin{aligned} S_{LOAD} &= 636 \angle 33.8^\circ \\ &\text{kVA} \end{aligned}$$

$$V_{LOAD} = 2200 \angle 0$$

$$V_{LOAD} I_{LOAD}^* = S_{LOAD} \quad I_{LOAD}^* = \frac{636000 \angle 33.8^\circ}{2200}$$

$$I_{LOAD} = 96.4 \angle -33.8^\circ \text{ A}$$

$$V_{SOURCE} = (0.4 + j2.7)(96.4 \angle -33.8^\circ) + 2200$$

$$2.73 \angle 81.6^\circ \cdot 96.4 \angle -33.8^\circ$$

$$263 \angle 47.8^\circ$$

$$= 176.7 + j194.8 + 2200$$

$$= 2377 + j194.8 = 2385 \angle 4.7^\circ$$

2.44, cont.

4/7

Source Power ?

$$V_{\text{source}} I_{\text{source}}^* = (2385 \angle 4.7) (96.4 \angle -33.8)^* \quad 1\phi$$

$$= 230 \angle 38.5 = 180 + j 143$$

kVA kW kVAR
 1 ϕ 1 ϕ

Load P was $528 \text{ kW } 3\phi = 176 \text{ kW } 1\phi$

Q $354 \text{ kVAR } 3\phi = 118 \text{ kVAR } 1\phi$

$$|I|^2 R = (96.4)^2 (0.4) = 3.72 \text{ kW } 1\phi$$

$$|I|^2 X = (96.4)^2 (2.7) = 25.1 \text{ kVAR } 1\phi$$

P Q



LOAD	176	118
------	-----	-----

LOSS	+ 3.7	25
------	-------	----


SOURCE	180 kW	143 kVAR
	1 ϕ	1 ϕ

Checks!

5/7

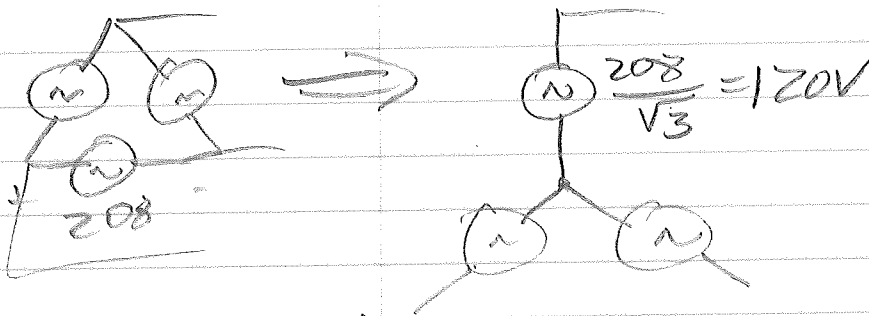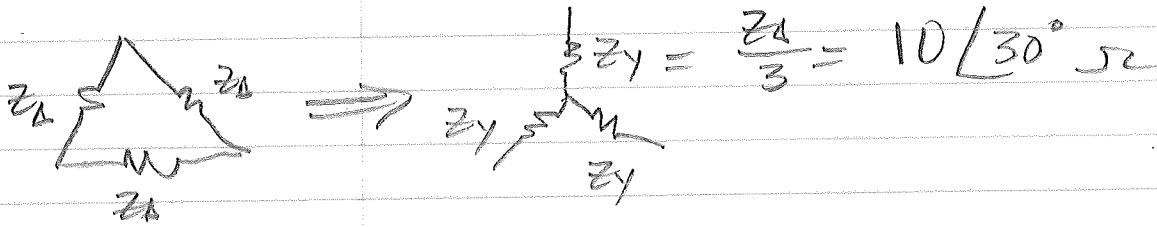2.46. Balanced, Convert Δ 's to Y's


One-line diagram for phase a.

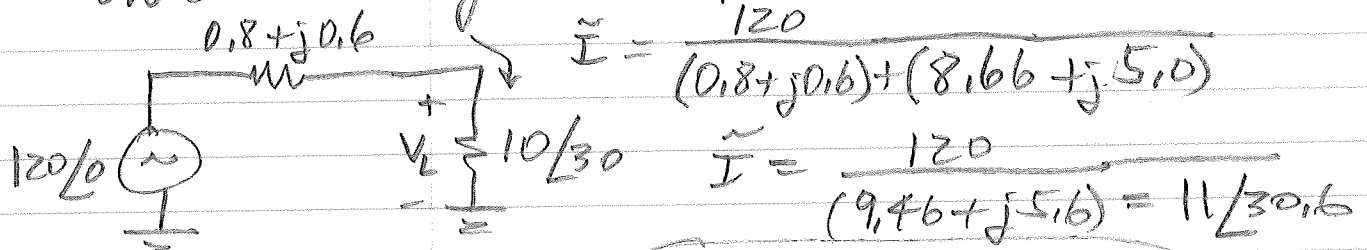

$$\tilde{I} = 10.92 \angle -30.6^\circ \text{ A}$$

$$\tilde{V}_L = (10.92 \angle -30.6^\circ)(10 \angle 30^\circ) =$$

$$\tilde{V}_L = 109.2 \angle -0.6^\circ \text{ V} \quad \text{Line to neutral}$$

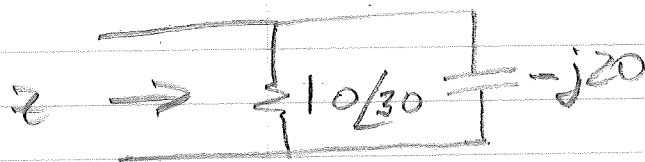Cap bank $Z_A = -j60 \Omega$, Wye equiv. = $-j20 \Omega$ 


$$Z = \frac{(10 \angle 30^\circ)(20 \angle -90^\circ)}{10 \angle 30^\circ - j20}$$

$$Z = \frac{200 \angle -60^\circ}{(8.66 + j5.0 - j20)} = \frac{200 \angle -60^\circ}{8.66 - j15} = \frac{200 \angle -60^\circ}{17.32 \angle -60^\circ}$$

$$Z = 11.55 \angle 0^\circ \quad (\text{perfect power factor correction})$$

$$V_{\text{Load}} = 120 \angle 0^\circ \left[\frac{11.55}{(0.8 + j0.6) + 11.55} \right] = 120 \angle 0^\circ \left[\frac{11.55}{12.36 \angle 2.8^\circ} \right] = 112.1 \angle -2.8^\circ \text{ Line-to-neutral}$$

Loss drop to load

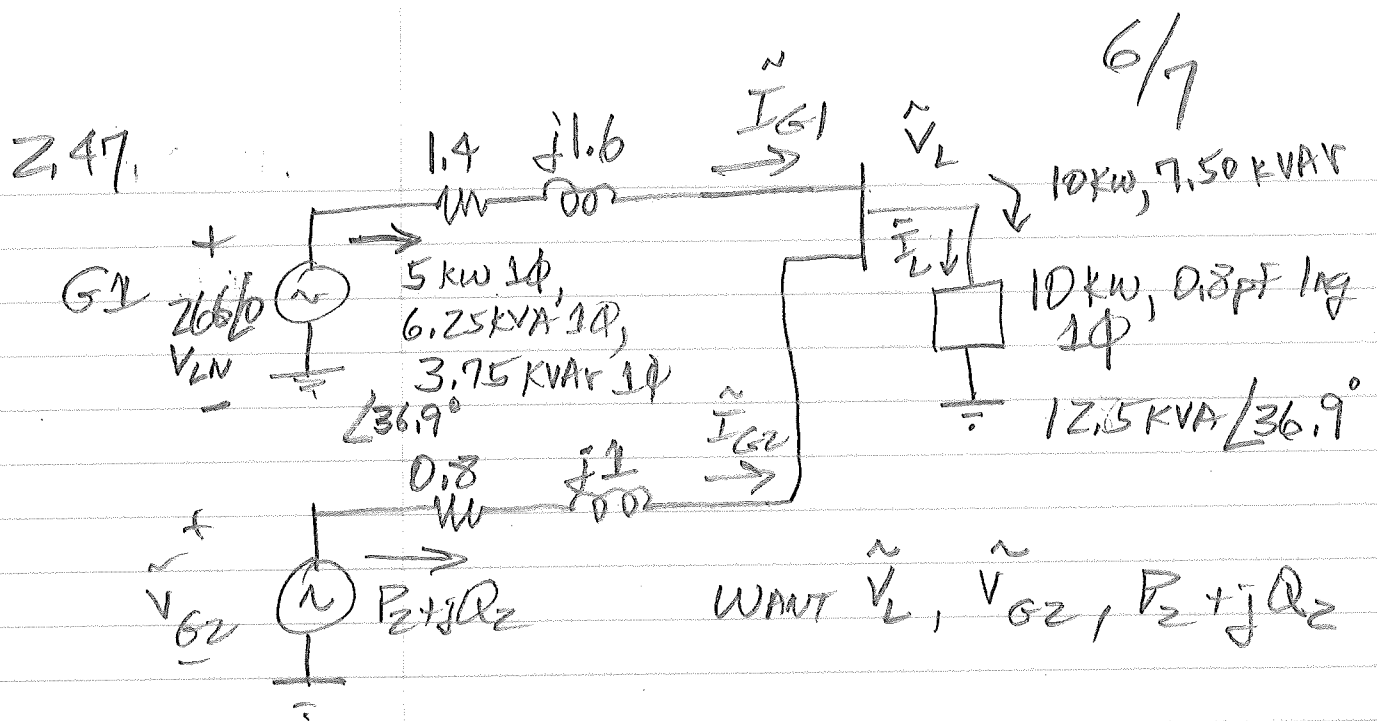

Strategy to solving this puzzle - start with what u know
 Conditions at G1 allow you to get $\tilde{I}_{G1}$

Voltage drop on line 1 gets you $\tilde{V}_L$

$\tilde{V}_L$ and $P_L + jQ_L$ gets you $\tilde{I}_L$

$\tilde{I}_L + \tilde{I}_{G1}$ gets you $\tilde{I}_{G2}$

$\tilde{I}_{G2}^2 (0.8)$ gets you P_{loss}
 (1) " " Q_{loss2}

Voltage drop on line 2 gets you $\tilde{V}_{G2}$

$\tilde{V}_{G2} \tilde{I}_{G2}^*$ gets you $P_2 + jQ_2$

$$\tilde{V}_{G1} \tilde{I}_{G1}^* = 6250 \angle 36.9^\circ, \tilde{I}_{G1} = \frac{6250 \angle -36.9^\circ}{266} = \boxed{\tilde{I}_{G1} = 23.5 \angle -36.9^\circ \text{ A}}$$

$$\tilde{V}_{drop} = (23.5 \angle -36.9^\circ)(1.4 + j1.6) = 50.0 \angle 11.9^\circ \text{ V}$$

$$2.13 \angle 48.8^\circ = 48.9 + j10.3 \text{ V}$$

7/7

2.49, cont

$$\hat{V}_{LOAD} = \hat{V}_{G1} = \hat{V}_{DAPP} = 266 - 48.9 - j10.3 = 217.1 - j10.3$$

$$\hat{V}_{LOAD} = 217.3 \angle -2.7^\circ \text{ V}$$

$$\hat{I}_{LOAD}^* = \frac{12500 \angle 36.9^\circ}{217.3 \angle -2.7^\circ} = 57.5 \angle 39.6^\circ, \hat{I}_{LOAD} = 57.5 \angle -39.6^\circ$$

$$\begin{aligned} \hat{I}_{G2} &= \hat{I}_L - \hat{I}_{G1} = (44.3 - j36.7) - (18.79 - j14.11) \\ &= 25.5 - j22.6 = 34.1 \angle -41.5^\circ \end{aligned}$$

$$\hat{V}_{G2} = \hat{V}_L + \hat{I}_{G2} (0.8 + j1) = 217.3 \angle -2.7^\circ + (34.1 \angle -41.5^\circ)(1.281 \angle 51.3^\circ)$$

$$43.7 \angle 9.8^\circ$$

$$= (217.1 - j10.24) + (43.1 + j7.44)$$

$$\hat{V}_{G2} = 260 - j2.8 = 260 \angle -0.6^\circ \text{ V}$$

$$\begin{aligned} V_{G2} I_{G2}^* &= (260 \angle -0.6^\circ)(34.1 \angle +41.5^\circ) = 8666 \angle 40.9^\circ \text{ VA} \\ &= 6550 \text{ W}, 5674 \text{ W} \end{aligned}$$

Power Check

Input	P	Q
G1	5000	3750
G2	6550	5674
	<u>11550</u>	<u>9424</u>

Load + Loss	P	Q
	10000	7500
	773	884
	<u>930</u>	<u>1163</u>
	11703	9547

Load	P	Q
	10000	7500

Loss	P	Q
Line 1	$(23.5)^2 (1.4)$ = 773	$(23.5)^2 (1.6)$ = 884
Line 2	$(34.1)^2 (0.8)$ = 930	$(34.1)^2 (1)$ = 1163

• Round off?