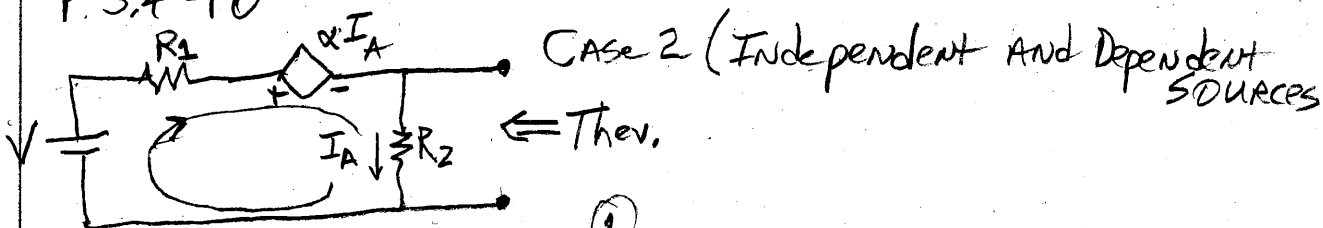


P.5.4-10




Find V_{OC} with both SOURCES ON. A loop Equation is simplest

① KVL. $-V + R_1 I_A + \alpha I_A + R_2 I_A = 0$
 $(R_1 + \alpha + R_2) I_A = V$


② You CAN see that $V_{OC} = I_A R_2 = \left(\frac{V}{R_1 + \alpha + R_2} \right) R_2$

So, $V_{OC} = V \left[\frac{R_2}{R_1 + \alpha + R_2} \right] V_{THEV}$

Now, find I_{SC} with both SOURCES ON.

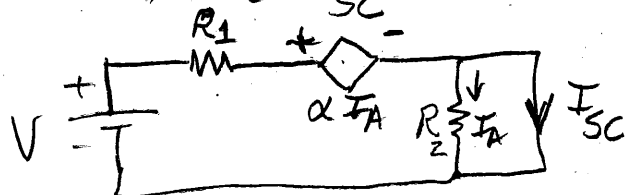

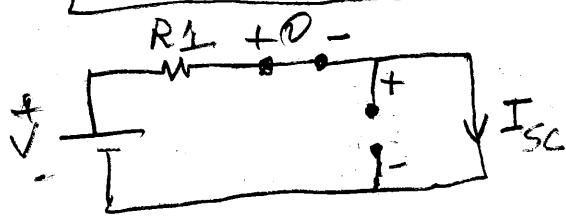
Since the voltage across R_2 is zero, then $I_A = 0$, and $\alpha I_A = 0$



So $I_{SC} = \frac{V}{R_1}$ Amps


$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{V \left[\frac{R_2}{R_1 + \alpha + R_2} \right]}{\frac{V}{R_1}}$

The Theveninck+ is

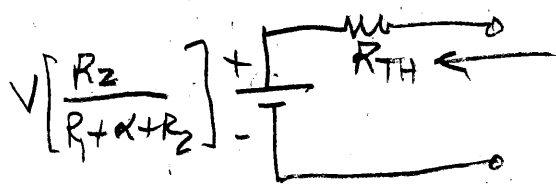

$R_{TH} = \frac{(R_1)(R_2)}{R_1 + \alpha + R_2} \Omega$

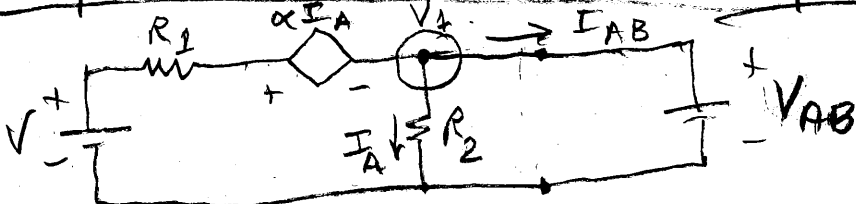COMPARE TO FICTITIOUS SOURCE METHOD, CASE 3



KCL, $\frac{(V_1 + \alpha I_A) - V}{R_1} + I_{AB} + I_A = 0$

Use $I_A = \frac{V_1}{R_2}$, $\frac{(V_1 + \alpha \frac{V_1}{R_2}) - V}{R_1} + I_{AB} + \frac{V_1}{R_2} = 0$

5.4-10, cont.

Get V_1 terms on one side

$$\frac{V_2 \left(1 + \frac{\alpha}{R_2}\right) - V}{R_1} + I_{AB} + \frac{V_1}{R_2} = 0$$

$$\frac{V_1 \left(1 + \frac{\alpha}{R_2}\right)}{R_1} + \frac{V_1}{R_2} - \frac{V}{R_1} + I_{AB} = 0$$

$$V_1 \left[\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2} \right] - \frac{V}{R_1} + I_{AB} = 0$$

Now, from the circuit, $V_1 \equiv V_{AB}$

$$V_{AB} \left[\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2} \right] = \frac{V}{R_1} - I_{AB}$$


$$V_{AB} = \frac{V}{R_1 \left[\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2} \right]} - \left[\frac{1}{\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2}} \right] I_{AB}$$

$$V_{AB} = V_{TH} - [R_{TH}] I_{AB}$$


$$R_{TH} = \frac{1}{\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2}} = \frac{R_1}{1 + \frac{\alpha}{R_2} + \frac{R_1}{R_2}} = \frac{(R_1)(R_2)}{R_2 + \alpha + R_1} \quad \left[\begin{array}{l} \text{Matches} \\ \text{Case 2} \end{array} \right]$$

$$V_{TH} = \frac{V}{R_1} \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_1 R_2} + \frac{1}{R_2}} = V \left[\frac{R_{TH}}{R_1} \right] = V \left[\frac{R_2}{R_1 + \alpha + R_2} \right] \quad \left[\begin{array}{l} \text{Matches} \\ \text{Case 2} \end{array} \right]$$

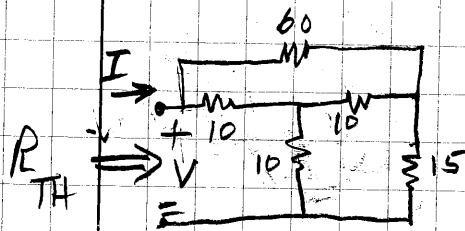Prob. 5.8-1. No Pspice. Reduce the right half to one Resistor. Then solve for the numbers



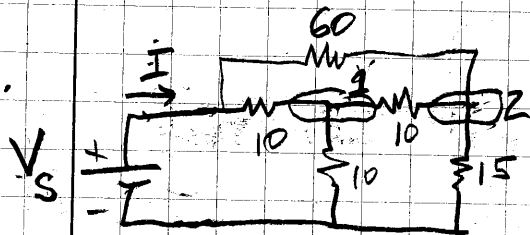Find V_{TH} - Apply a voltage on the left, find the current, then $R_{TH} = \frac{V}{I}$



$$\textcircled{1} \frac{V_1 - V_S}{10} + \frac{V_1 - V_2}{10} + \frac{V_1}{10} = 0, \textcircled{2} \frac{V_2 - V_1}{10} + \frac{V_2 - V_S}{60} + \frac{V_2}{15} = 0$$

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{10} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} - \frac{1}{60} & \frac{1}{10} + \frac{1}{60} + \frac{1}{15} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_S}{10} \\ \frac{V_S}{60} \end{bmatrix}$$

$$\times 60 \quad \begin{bmatrix} 6+6+6 & -6 \\ -6-1 & 6+1+4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6V_S \\ 1V_S \end{bmatrix}, \quad \begin{bmatrix} 18 & -6 \\ -7 & 11 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6V_S \\ 1V_S \end{bmatrix}$$

$$\begin{cases} 18V_1 - 6V_2 = 6V_S \\ -7V_1 + 11V_2 = 1V_S \end{cases}, \quad V_2 = \frac{V_S + 7V_1}{11}$$

$$18V_1 - 6 \left[\frac{7V_1 + 1V_S}{11} \right] = 6V_S$$

$$3V_1 - \left[\frac{7V_1 + 1V_S}{11} \right] = 1V_S$$

$$V_1 \left[3 - \frac{7}{11} \right] = \left(1 + \frac{1}{11} \right) V_S$$

$$V_1 \left[\frac{26}{11} \right] = \left[\frac{12}{11} \right] V_S$$

$$V_1 = \frac{12}{26} V_S = \frac{6}{13} V_S$$

$$V_2 = \frac{7}{11} V_1 + \frac{V_S}{11}$$

$$V_2 = \frac{7}{11} \left(\frac{6}{13} \right) V_S + \frac{V_S}{11}$$

$$11V_2 = \frac{42}{13} V_S + V_S$$

$$11V_2 = \frac{1}{13} (42V_S + 13V_S)$$

$$11V_2 = \frac{55}{13} V_S, \quad V_2 = \frac{5}{13} V_S$$


FROM CKT

$$I = \frac{V_S - V_1}{10} + \frac{V_S - V_2}{60} = \frac{V_S - \frac{6}{13} V_S}{10} + \frac{V_S - \frac{5}{13} V_S}{60}$$


$$I = V_S \left[\frac{7/13}{10} + \frac{8/13}{60} \right] = V_S \left(\frac{1}{13} \right) \left(\frac{7}{10} + \frac{8}{60} \right) = V_S \left(\frac{1}{13} \right) \left(\frac{42+8}{60} \right) = V_S \left(\frac{1}{13} \right) \left(\frac{5}{6} \right)$$

$$= V_S \left(\frac{5}{78} \right), \quad R = \frac{78}{5} = 15.6 \, \Omega$$

HW#12
5.8-1 (LEFT-HAND SIDE)

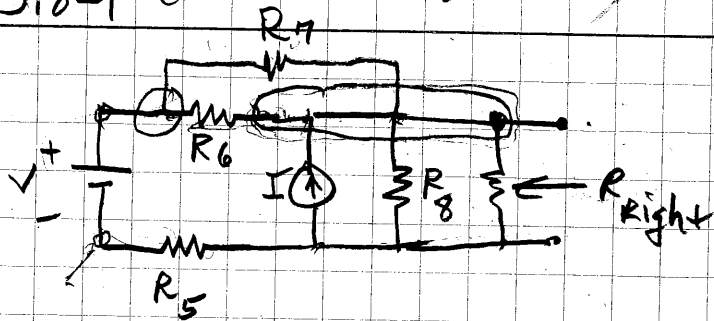


P. 5.4-15

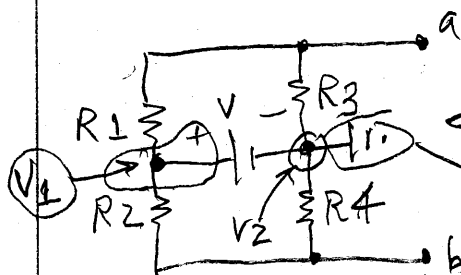

Case 1, $V_{TH} = V_{OC}$
TURN off sources,
Find R_{ab}

GND Reference,
NO current in it.

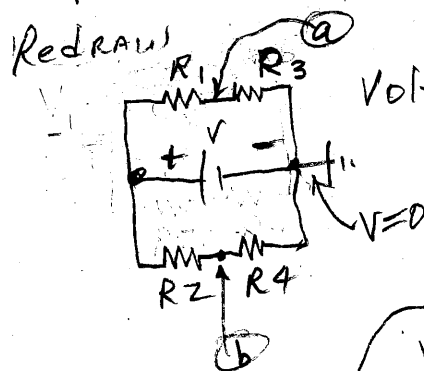

Voltage divider on top and bottom


$$V_a = V \left[\frac{R_3}{R_1 + R_3} \right]$$

$$V_b = V \left[\frac{R_4}{R_2 + R_4} \right]$$

$$V_a - V_b = V \left[\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right] = V_{OC} = V_{TH}$$

CAN'T simplify

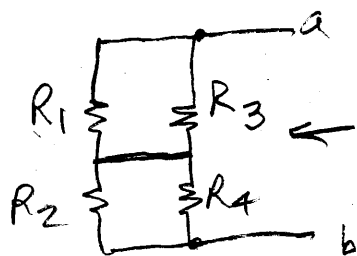Now, turn
off the sources
and find R_{ab}



$$R_{ab} = [R_1 || R_3] + [R_2 || R_4]$$

$$= \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} = R_{THEV}$$

CAN'T simplify