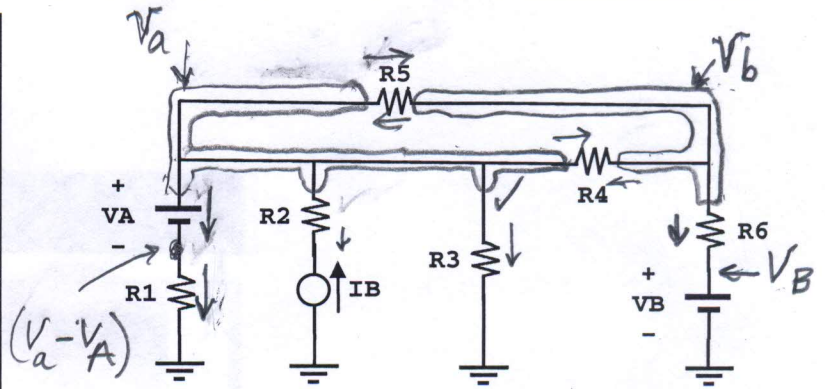


Problem 1

- Using Nodal Analysis, identify the major nodes and super nodes, name them V_a , V_b , V_c , etc., using lower case a,b,c.
- Carefully draw a closed loop around each one's full equipotential range of connections.
- Develop the equations needed to solve the circuit in the boxes below, one node per box.
- Place the equations into the empty matrix below, starting at top-left.



Eq. for Node a. $\frac{(V_a - V_A)}{R_1} + \frac{(V_a - V_b)}{R_5} + \frac{(V_a - V_b)}{R_4} + \frac{V_a}{R_3} + I_B = 0$


Eq. for Node b. $\frac{V_b - V_B}{R_6} + \frac{V_b - V_a}{R_4} + \frac{V_b - V_a}{R_5} = 0$

Eq. for Node ____.

Eq. for Node ____.

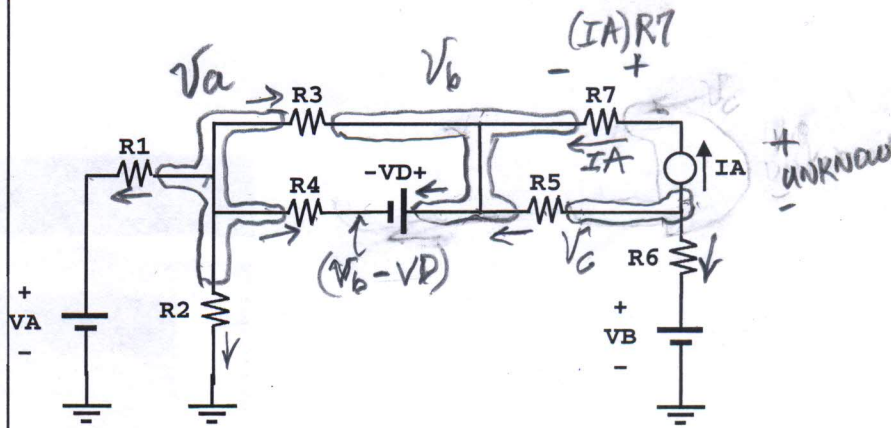Problem 1

- Using Nodal Analysis, identify the major nodes and super nodes, name them V_a , V_b , V_c , etc., using lower case a,b,c.
- Carefully draw a closed loop around each one's full equipotential range of connections.
- Develop the equations needed to solve the circuit in the boxes below, one node per box.
- Place the equations into the empty matrix below, starting at top-left.




Eq. for Node a. $\frac{V_a}{R_2} + \frac{(V_a - V_A)}{R_1} + \frac{(V_a - V_b)}{R_3} + \frac{[V_a - (V_b - V_D)]}{R_4}$

Eq. for Node b. $\frac{(V_b - V_D) - V_a}{R_4} + \frac{V_b - V_a}{R_3} - I_A + \frac{V_b - V_c}{R_5} = 0$

Eq. for Node c. $\frac{V_c - V_b}{R_5} + I_A + \frac{V_c - V_B}{R_6} = 0$

Eq. for Node ____.

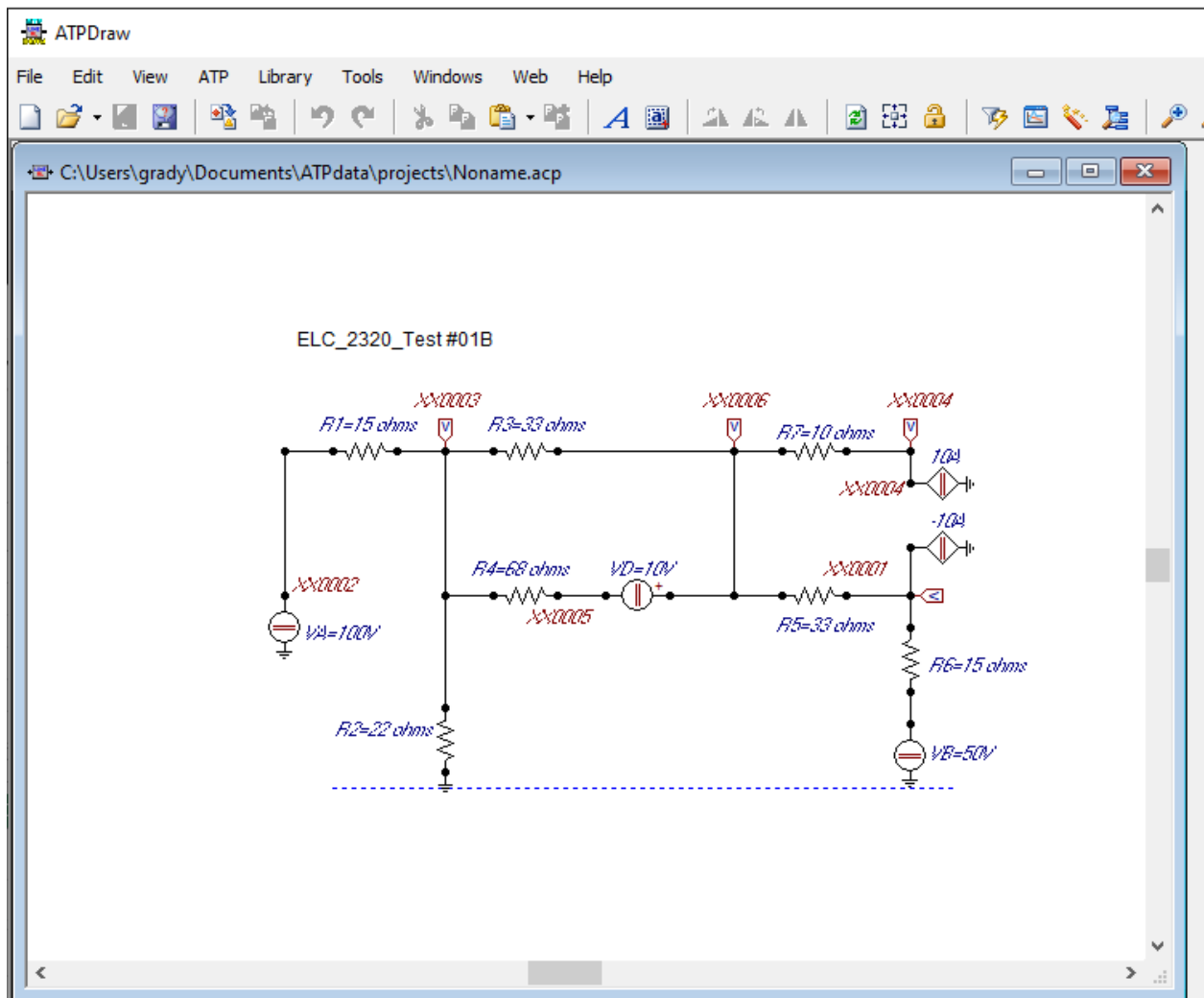

noname.csv

File Home Insert New Draw Page Form Data Review View

AutoSave Off

A1 Time

	A	B	C	D	E
1	Time	Voltage	Voltage	Voltage	Voltage
2	Second	XX0003	XX0006	XX0001	XX0004
3					
4	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
5	1.00E-03	9.52E+01	1.88E+02	-1.01E+01	2.88E+02
6	2.00E-03	9.52E+01	1.88E+02	-1.01E+01	2.88E+02

noname

Ready 100%