

P 10.5-9 Figure P 10.5-9 shows an ac circuit represented in both the time domain and the frequency domain. Suppose

$$Z_1 = 15.3 \angle -24.1^\circ \Omega \text{ and } Z_2 = 14.4 \angle 53.1^\circ \Omega$$

Determine the voltage $v(t)$ and the values of R_1 , R_2 , L , and C .

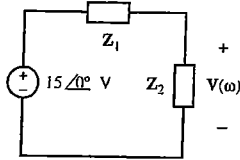
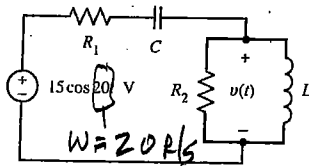


Figure P 10.5-9

HW 18, #1, Due Wed 4/21

ω Radians/sec for this circuit is 20. $\text{Freq (Hz)} = \frac{\omega}{2\pi}$

$$Z_1 \text{ is } R_1 + \frac{1}{j\omega C}$$

$$Z_2 \text{ is } R_2 \parallel j\omega L = \frac{(R_2)(j\omega L)}{R_2 + j\omega L}$$

$$Z_1 = 15 \angle -24.1^\circ = 15 \cos(-24.1^\circ) + j15 \sin(-24.1^\circ)$$

$$\leftarrow R_1 + jX, X = \frac{1}{j\omega C}$$

$$\text{so } R_1 = 13.69 \Omega$$

$$X = 15(-0.4083) = -6.125$$

$$jX = -j6.125 \Omega$$

$$jX = \frac{1}{j\omega C} = -j6.125$$

$$\rightarrow \frac{1}{\omega C} = 6.125, \omega C = \frac{1}{6.125}, C = \frac{1}{6.125(20)} = 0.0082 \text{ F}$$

$$\text{Check } \frac{1}{\omega C} = \frac{1}{(20)(8.163 \times 10^{-6})} = 6.125$$

$$C = 8.163 \mu\text{F}$$

$$Z_2 = 14.4 \angle 53.1^\circ = 14.4 [\cos(53.1^\circ) + j\sin(53.1^\circ)] = 8.646 + j11.52$$

$$\text{Check } \sqrt{(8.646)^2 + (11.52)^2} = 14.40 \checkmark$$

$$\text{Define } Y_2 = \frac{1}{Z_2}$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R_2} + \frac{1}{j\omega L} = \frac{1}{14.4 \angle 53.1^\circ} = \frac{1 \angle -53.1^\circ}{14.4}$$


$$Y_2 = 0.0694 \angle -53.1^\circ = 0.0694 [\cos(-53.1^\circ) + j\sin(-53.1^\circ)]$$

$$Y_2 = 0.0694 [0.600 - j0.800] = 0.04164 - j0.0555$$

So Real part of Y_2 is 0.04164, Imag part of Y_2 is $-j0.0555$

$$\text{So } R_2 = \frac{1}{0.04164} = 24.0 \Omega, \frac{1}{j\omega L} = -j0.0555, 0.0555\omega L = 1, L = \frac{1}{0.0555(20)} = 0.901 \text{ H}$$
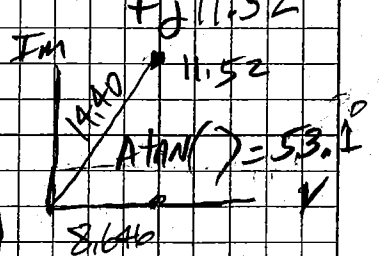
$$\text{Check } R \parallel j\omega L = \frac{j\omega RL}{R + j\omega L} = \frac{j(20)(24)(0.901)}{24 + j18.02} = \frac{j432.5}{30 \angle 36.9^\circ} = 14.4 \angle -53.1^\circ$$



P 10.5-18 Determine the steady-state current $i(t)$ for the circuit shown in Figure P 10.5-18.

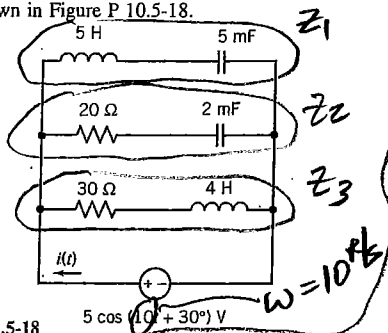


Figure P 10.5-18

$$5 \angle 30^\circ \text{ V} \omega = 10 \text{ rad/s}$$

#W18, #2


$$Z_1 = j\omega 5 + \frac{1}{j\omega (5 \times 10^{-3})} = j\omega 5 - j \left[\frac{200}{\omega} \right] = j50 - j20 = j30 \Omega = 30 \angle 90^\circ$$

$$Z_2 = 20 + \frac{1}{j\omega (2 \times 10^{-3})} = 20 - j \left[\frac{0.5 \times 10^3 = 500}{\omega} \right] = 20 - j50 = 53.9 \angle -68.2^\circ$$

$$Z_3 = 30 + j\omega 4 = 30 + j40 = 50 \angle 53.1^\circ$$

Convert each Z to polar form and find the current passing through each Z
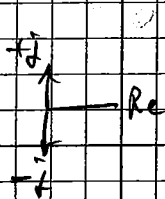
$$Z_1 = 30 \angle 90^\circ, Z_2 = \sqrt{20^2 + 50^2} \angle \tan^{-1} \frac{-50}{20} = 53.9 \angle -68.2^\circ$$



$$\tilde{I}_{TOT} = \left[\frac{5 \angle 30^\circ}{30 \angle 90^\circ} + \frac{5 \angle 30^\circ}{53.9 \angle -68.2^\circ} + \frac{5 \angle 30^\circ}{50 \angle 53.1^\circ} \right] = 0.1667 \angle (30-90) + 0.0928 \angle (30+68.2) + 0.100 \angle (30-53.1)$$

$$\tilde{I}_{TOT} = 0.1667 \angle -60^\circ + 0.0928 \angle 98.2^\circ + 0.1 \angle -23.1^\circ$$

$$0.0834 - j0.1444 - 0.0132 + j0.0919 + 0.09198 - j0.03923$$

$$= 0.1662 - j0.0917 = \sqrt{0.1662^2 + 0.0917^2} \angle \tan^{-1} \left(\frac{-0.0917}{0.1662} \right)$$

$$I_{TOT} = 0.1897 \angle -28.9^\circ \text{ A}$$

P 10.5-19 Determine the steady-state voltage $v(t)$ for the circuit shown in Figure P 10.5-19.

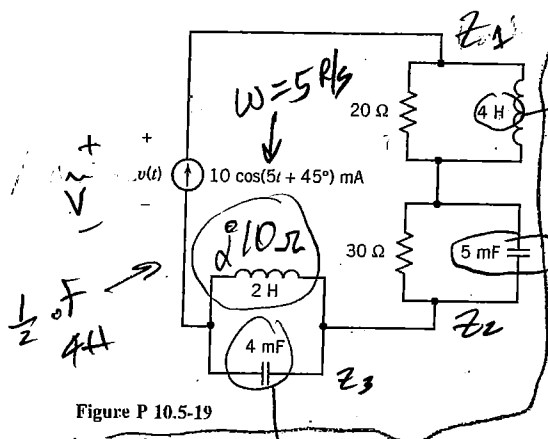


Figure P 10.5-19

HW 18, #3

$$j\omega L = j20 \Omega$$

$$\frac{1}{j\omega(5 \times 10^{-3})} = \frac{0.2 \times 10^3}{j5} = -j \frac{200}{5} = -j40 \Omega$$

5/4 ratio

$$\frac{1}{j\omega(4 \times 10^{-3})} = \frac{0.25 \times 10^3}{j40} = -j \frac{250}{40} = -j6.25 \Omega$$

$$Z_1 = 20 \Omega \parallel j20 = \frac{20(j20)}{20 + j20} = \frac{j20}{1 + j} = \frac{20 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = \frac{20}{\sqrt{2}} \angle 45^\circ \Omega$$

$$Z_2 = 30 \Omega \parallel (-j40) = \frac{30(-j40)}{30 - j40} = \frac{-j1200}{50 \angle -53.1^\circ} = \frac{1200 \angle -90^\circ}{50 \angle -53.1^\circ} = 24 \angle -36.9^\circ \Omega$$

$$Z_2 = 24 \angle -36.9^\circ \Omega$$

$$Z_3 = j10 \parallel (-j50) = \frac{(j10)(-j50)}{j10 - j50} = \frac{500}{-j40} = \frac{j500}{40} = j12.5 \Omega$$

$$\text{KVL: } -\tilde{V} + 10 \angle 45^\circ \text{ Amps} [Z_1 + Z_2 + Z_3] = 0$$

$$\tilde{V} = 10 \angle 45^\circ [Z_1 + Z_2 + Z_3] = \frac{20}{\sqrt{2}} \angle 45^\circ + 24 \angle -36.9^\circ + 12.5 \angle 90^\circ$$

$$\tilde{V} = \left[\begin{matrix} 0.01 \angle 45^\circ \\ \text{Amps} \end{matrix} \right] \left[\begin{matrix} 124 \angle 16.4^\circ \end{matrix} \right] = 1.24 \angle 121.4^\circ$$

$$\begin{aligned} &= 14.14(0.7071 + j0.7071) + 24(0.800 - j0.600) + j12.5 \\ \text{Gather terms } (Z_1 + Z_2 + Z_3) &= [10 + j19.2] + j[10 - 14.4] + 12.5 \\ &= 29.2 + j120.6 \Omega \\ &= 124.1 \angle 76.4^\circ \end{aligned}$$

P 10.5-24 $\oplus$ When the switch in the circuit shown in Figure P 10.5-24 is open and the circuit is at steady state, the capacitor voltage is

$$v(t) = 14.14 \cos(100t - 45^\circ) \text{ V}$$

When the switch is closed and the circuit is at steady state, the capacitor voltage is

$$v(t) = 17.89 \cos(100t - 26.6^\circ) \text{ V}$$

Determine the values of the resistances R_1 and R_2 .


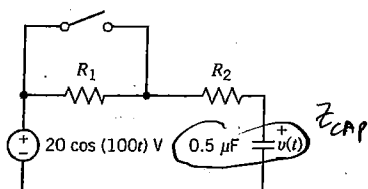


Figure P 10.5-24


HW 18, #4

$$Z_{\text{cap}} = \frac{1}{j\omega C} = \frac{1}{j(100)(0.5 \times 10^{-6})}$$
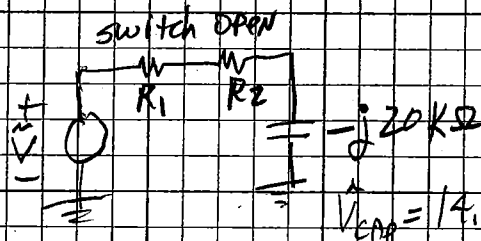
$$Z_{\text{cap}} = \frac{10^6}{j50} = \frac{100 \times 10^4}{j50} = -j20000 = -j20 \text{ k}\Omega$$



Switch Open

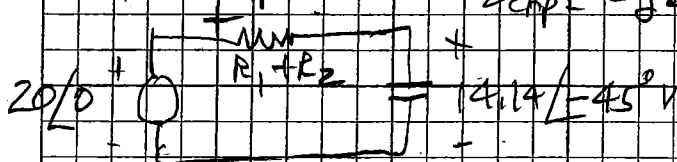

$$Z_{\text{cap}} = -j20 \text{ k}\Omega$$

$$I_{\text{cap}} = \frac{14.14 / -45^\circ}{20 \text{ k}\Omega / -90^\circ}$$

$$I_{\text{cap}} = I_{\text{loop}}$$

$$= 0.707 / 45^\circ \text{ mA}$$

minus

milliamps

$$\text{Now } V_{\frac{R_1 R_2}{\text{both}}} = [20 / 0 - 14.14 / -45^\circ] = I_{\text{cap}} (R_1 + R_2)$$

$$(R_1 + R_2) = \frac{V_{\frac{R_1 R_2}{\text{both}}}}{I_{\text{cap}}} = \frac{20 - [10 - j10]}{0.707 / 45^\circ \text{ mA}} = \frac{10 + j10}{0.707 / 45^\circ}$$

Now R_1 is shorted

$$V_{\text{cap}} = 17.89 / -26.6^\circ$$

$$I_{\text{cap}} = \frac{17.89 / -26.6^\circ}{-j20 \text{ k}\Omega} = \frac{17.89 / -26.6^\circ}{20 \text{ k}\Omega / -90^\circ}$$

$$R_1 + R_2 = 20 \text{ k}\Omega$$

$$I_{\text{cap}} = 0.895 \text{ mA} / 63.4^\circ$$

$$\text{Now, we have that } V_{\text{source}} - V_{\text{cap}} = V_{R_2} = 20 / 0 - 17.89 / -26.6^\circ$$

$$V_{R_2} = [20 - [16.0 - j8.0]] = [4 + j8] \text{ Volts} = 8.94 / 63.4^\circ$$

$$R = \frac{V_{R_2}}{I_{\text{cap}}} = \frac{8.94 / 63.4^\circ}{0.895 \text{ mA} / 63.4^\circ} = 10 \text{ k}\Omega, \text{ so } R_1 \text{ \& } R_2 \text{ are each } 10 \text{ k}\Omega$$

P 10.8-6 The inputs to the circuit shown in Figure P 10.8-6 are

$$v_{s1}(t) = 30 \cos(20t + 70^\circ) \text{ V}$$

and

$$v_{s2}(t) = 18 \cos(10t - 15^\circ) \text{ V}$$

The response of this circuit is the current $i(t)$. Determine the steady-state response of the circuit.

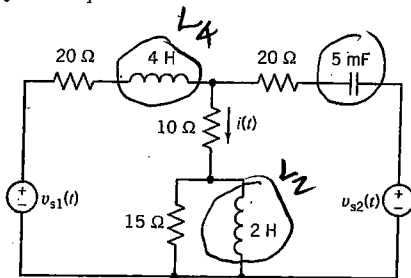


Figure P 10.8-6

HW 18, #5

Use SUPERPOSITION, ONE SOURCE AT A TIME


Step 1, v_{s1} ON, v_{s2} OFF (shorted)

v_{s1} is 20 r/s

$$j\omega L_4 = j80 \Omega, j\omega L_2 = j40 \Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j(20)(5 \times 10^{-3})} = \frac{1000}{j100}$$

$$= -j10 \Omega$$

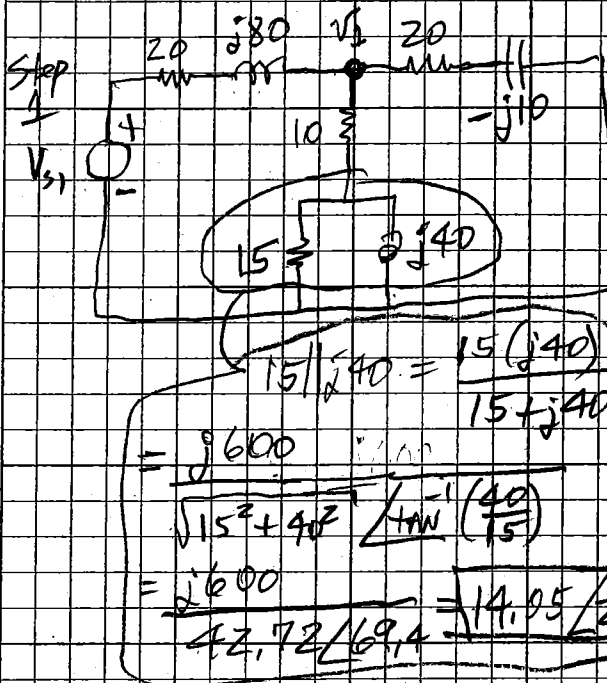

$$\text{KCL} \quad \frac{V_1 - V_{s1}}{20 + j80} + \frac{V_1}{20 - j10} + \frac{V_1}{10 + 14.05 \angle 20.6^\circ} = 0$$

Solve for V_1 ,

$$\text{Then } I = \frac{V_1}{10 + 14.05 \angle 20.6^\circ}$$

Then do Step 2. The Final Answer is Step 1 + Step 2

P 10.8-9 Using the principle of superposition, determine $i(t)$ of the circuit shown in Figure P 10.8-9 when $v_1 = 10 \cos(10t) \text{ V}$
 Answer: $i = -2 + 0.71 \cos(10t - 45^\circ) \text{ A}$

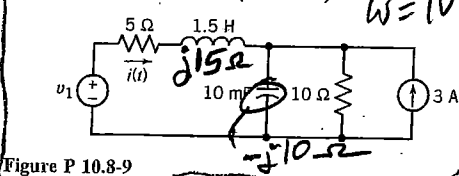


Figure P 10.8-9

HW 18, #6


$$1.5 \text{ H} \Rightarrow j\omega L = j(10)(1.5) = j15 \Omega$$

$$10 \text{ mF} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(10 \times 10^{-3})}$$

$$= \frac{10^3}{j(10)(10)} = \frac{1000}{j100}$$


$$= -j10 \Omega$$

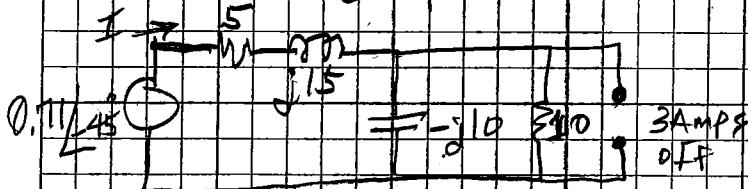For the AC ckt, turn off the 3A DC - Open ckt



The I will be $\frac{0.71 \angle -45^\circ}{5 + j15 + (-j10) \parallel (10)}$

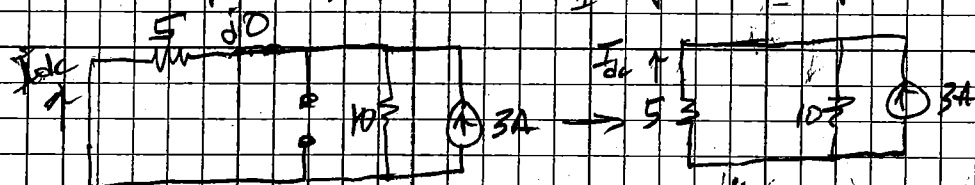For the DC problem, turn off v_1 by shorting it



$$10 \parallel 5 = 3.333 \Omega$$

$$3 \text{ A}(3.333 \Omega) = 10 \text{ V}$$

$$I_{dc} = -\frac{10}{5} = -2 \text{ A}$$

Now Add the two circuit results