
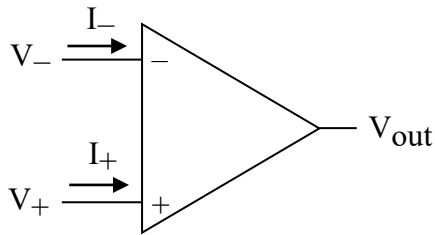


Op Amps

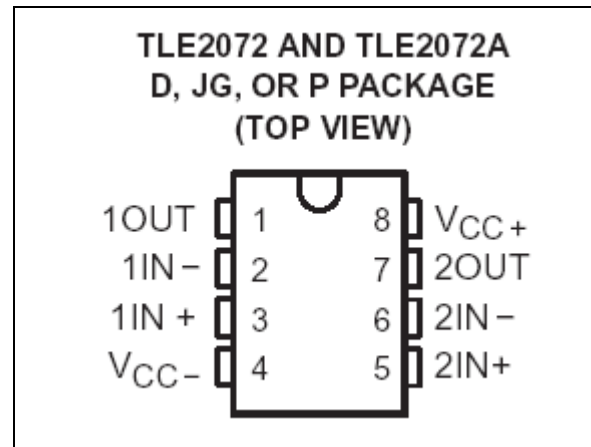


Assumptions for ideal op amp

- $V_{out} = K(V_+ - V_-)$, K large (hundreds of thousands, or one million).
- $I_+ = I_- = 0$.
- Voltages are with respect to power supply ground.
- Output current is not limited.



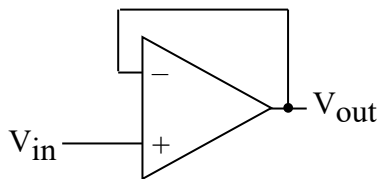Buffer Amplifier (converts high impedance signal to low impedance signal)




$$V_{out} = K(V_{in} - V_{out}), \text{ so } V_{out} + KV_{out} = KV_{in}, \text{ so}$$

$$V_{out}(1 + K) = KV_{in}, \text{ so } V_{out} = V_{in} \cdot \frac{K}{1 + K}. \text{ Since } K \text{ is}$$

large, then $V_{out} = V_{in}$.

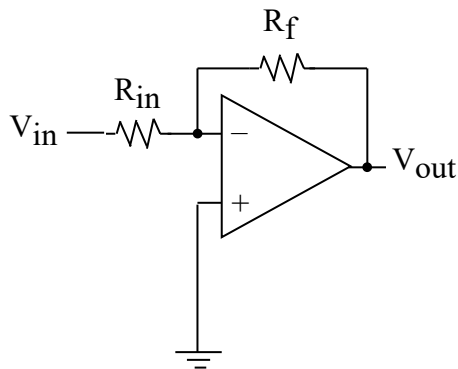Inverting Amplifier (used for proportional control signal)



$$V_{out} = K(0 - V_-) = -KV_-, \text{ so } V_- = -\frac{V_{out}}{K}.$$


$$\text{KCL at the } - \text{ node is } \frac{V_- - V_{in}}{R_{in}} + \frac{V_- - V_{out}}{R_f} = 0.$$

Eliminating V_- yields

$$-\frac{V_{out}}{K} - V_{in} + \frac{V_{out}}{K} - V_{out} = 0, \text{ so}$$

$$-V_{out} \left(\frac{1}{KR_{in}} + \frac{1}{KR_f} + \frac{1}{R_f} \right) = \frac{V_{in}}{R_{in}}. \text{ For large } K, \text{ then } \frac{-V_{out}}{R_f} = \frac{V_{in}}{R_{in}}, \text{ so } V_{out} = -V_{in} \frac{R_f}{R_{in}}.$$

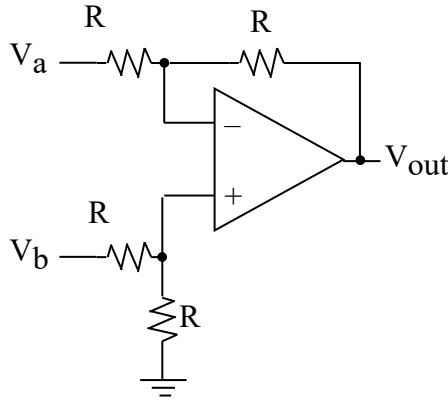Inverting Difference (used for error signal)



$$V_{out} = K(V_+ - V_-) = K\left(\frac{V_b}{2} - V_-\right), \text{ so}$$

$$V_- = \frac{V_b}{2} - \frac{V_{out}}{K}.$$

$$\text{KCL at the } - \text{ node is } \frac{V_- - V_a}{R} + \frac{V_- - V_{out}}{R} = 0, \text{ so}$$


$$V_- - V_a + V_- - V_{out} = 0, \text{ yielding } V_- = \frac{V_a + V_{out}}{2}.$$

Eliminating V_- yields

$$V_{out} = K\left(\frac{V_b}{2} - \frac{V_a + V_{out}}{2}\right), \text{ so } V_{out} + K \frac{V_{out}}{2} = K\left(\frac{V_b - V_a}{2}\right), \text{ or } V_{out}\left(1 + \frac{K}{2}\right) = K\left(\frac{V_b - V_a}{2}\right).$$

For large K , then $V_{out} = -(V_a - V_b)$.

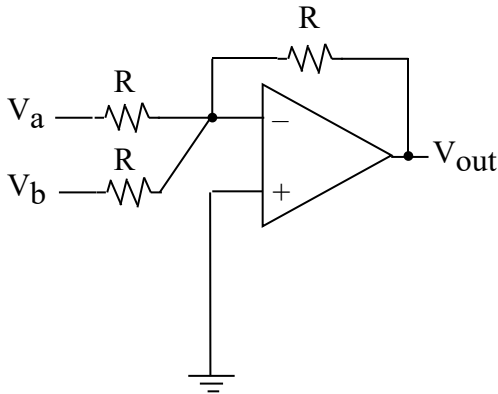Inverting Sum (used to sum proportional and integral control signals)



$$V_{out} = K(0 - V_-) = -KV_-, \text{ so } V_- = \frac{-V_{out}}{K}.$$

KCL at the $-$ node is


$$\frac{V_- - V_a}{R} + \frac{V_- - V_b}{R} + \frac{V_- - V_{out}}{R} = 0, \text{ so}$$

$$3V_- = V_a + V_b + V_{out}.$$

Substituting for V_- yields $3\left(\frac{-V_{out}}{K}\right) = V_a + V_b + V_{out}$, so $V_{out}\left(\frac{-3}{K} - 1\right) = V_a + V_b$.

Thus, for large K , $V_{out} = -(V_a + V_b)$

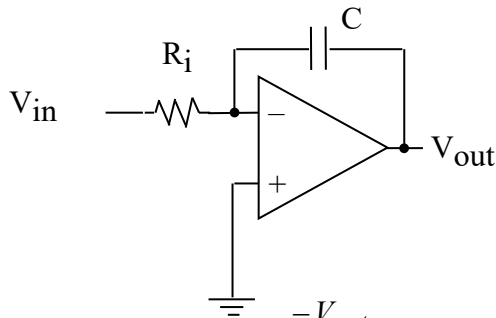Inverting Integrator (used for integral control signal)



$$V_{out} = K(V_+ - V_-) = K(0 - V_-), \text{ so}$$

$$V_- = -\frac{V_{out}}{K}. \text{ KCL at the } - \text{ node is}$$


$$\frac{V_- - V_{in}}{R_i} + C \frac{d}{dt}(V_- - V_{out}) = 0.$$

Eliminating V_- yields $\frac{-\frac{V_{out}}{K} - V_{in}}{R_i} + C \frac{d}{dt}\left(\frac{-V_{out}}{K} - V_{out}\right) = 0$. For large K ,

$$-C \frac{d}{dt} V_{out} = \frac{V_{in}}{R_i}, \text{ or } \frac{d}{dt} V_{out} = \frac{-V_{in}}{R_i C}. \text{ So } \boxed{V_{out} = \frac{-1}{R_i C} \int V_{in} dt.}$$

Lower R_i or C to increase integrator response.

Inverting Differentiator

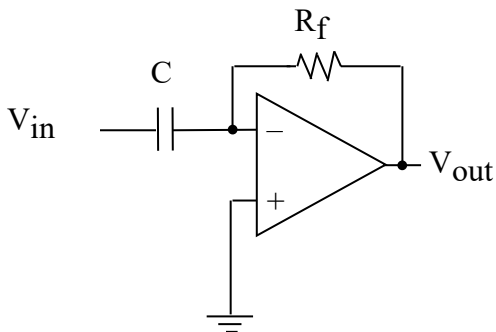

$$V_{out} = K(V_+ - V_-) = K(0 - V_-), \text{ so } V_- = -\frac{V_{out}}{K}.$$

KCL at the $-$ node is

$$\frac{V_- - V_{out}}{R_f} + C \frac{d}{dt}(V_- - V_{in}) = 0. \text{ Eliminating } V_-$$


yields

$$\frac{\frac{-V_{out}}{K} - V_{out}}{R_f} + C \frac{d}{dt}\left(\frac{-V_{out}}{K} - V_{in}\right) = 0. \text{ For large } K, \text{ we have } \frac{-V_{out}}{R_f} + C \frac{d}{dt}(-V_{in}) = 0, \text{ so}$$

$$\boxed{V_{out} = -R_f C \frac{dV_{in}}{dt}.}$$


Raise R_f or C to increase differentiator response.

Bandpass Filter

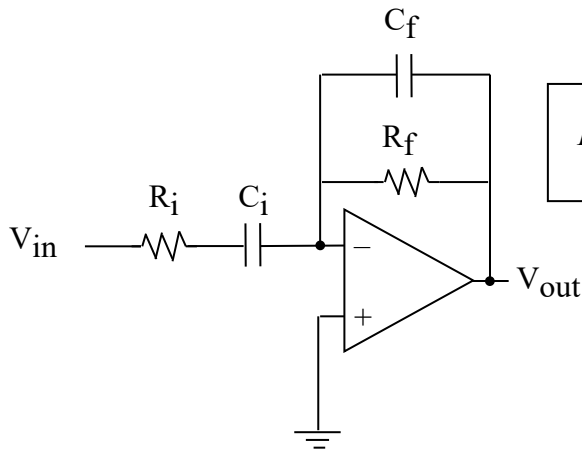

$$H(\omega) = -R_f C_i \frac{j\omega}{(1 + j\omega R_i C_i)(1 + j\omega R_f C_f)}$$

Butterworth Low-Pass

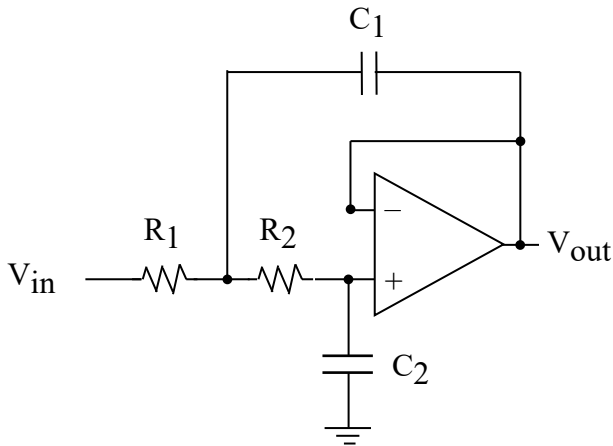

$$H(\omega) = \frac{1}{s^2 + 2\alpha s + \omega_o^2}$$

$$\alpha = \frac{R_1 + R_2}{2R_1 R_2 C_1}$$

$$\omega_o^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\zeta^2 = \frac{(R_1 + R_2)^2 C_2}{4R_1 R_2 C_1}$$

Place the denominator's breakpoint at ω_o . Let $R_1 = R_2$, which leads to $\zeta = \sqrt{\frac{C_2}{C_1}}$. It is clear that underdamped response requires $C_2 < C_1$. Substituting $R_1 = R_2$ into the equation for ω_o yields $R_1 = R_2 = \frac{1}{\omega_o \sqrt{C_1 C_2}}$.

If we want $f_o = 10\text{kHz}$, then $\omega_o = 2\pi \cdot 10\text{kHz}$. Selecting $C_1 = 0.01\ \mu\text{F}$ and $C_2 = 0.001\ \mu\text{F}$, then $R_1 = R_2$ should be approximately $5\ \text{k}\Omega$ (use parallel $10\ \text{k}\Omega$ resistors). The corresponding

$$\zeta = \sqrt{\frac{C_2}{C_1}} = 0.316.$$