

## TOPICS

### 1. Power Definitions and Equations. Why?

As with any other technology, the underlying physics must be understood so that equations and models can be developed that simulate actual behavior.

### 2. Three-Phase Power. Why?

Losses are minimized because there are no ground or neutral return currents. Also, three-phase machines are smaller and much more efficient than single-phase machines of the same power rating.

### 3. Transformer Models. Why?

To move power over long distances and minimize  $I^2R$  losses, transmission line voltages must be boosted to much higher levels than voltages produced by generators or required by end-users.

### 4. Per Unit System. Why?

To make modeling and simulation of circuits having transformers much easier. A by-product is that per-unitized equipment parameters such as ratings and impedances fall into narrow and predictable ranges.

### 5. Symmetrical Components. Why?

Greatly simplifies analysis of normal power system operation, as well as abnormal events such as unbalanced faults.

### 6. Transmission Line Models. Why?

Necessary for designing and simulating power systems for loadflow, short-circuit, and stability purposes.

### 7. Fault (Short-Circuit) Calculations and Voltage Sags. Why?

So that a power system can be properly protected by detecting and isolating faults within 0.1 second. 1 second is a very long time for a fault to exist - long enough to cause grid blackouts.

Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015

1

## 1. Power Definitions and Equations, cont.


As with any other technology, the underlying physics must be understood so that equations and models can be developed that simulate actual behavior.

### Instantaneous power $p(t)$ flowing into the box

$$v(t) = V \sin(\omega_o t + \delta),$$

$$i(t) = I \sin(\omega_o t + \theta)$$

$$p(t) = v(t) \bullet i(t)$$

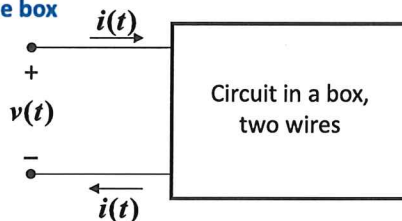

$$p(t) = v(t) \bullet i(t) = V \sin(\omega_o t + \delta) \bullet I \sin(\omega_o t + \theta)$$

$$p(t) = VI \left[ \frac{\cos(\delta - \theta) - \cancel{\cos(2\omega_o t + \delta + \theta)}}{2} \right]$$

zero average

$$P_{avg} = \frac{1}{T} \int_{t_o}^{t_o+T} p(t) dt = \frac{VI}{2} \cos(\delta - \theta) = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos(\delta - \theta)$$

peak  
rms

### Average power $P_{avg}$ flowing into the box

$$P_{avg} = V_{rms} I_{rms} \boxed{\cos(\delta - \theta)}$$

Power factor

Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015

2

## 1. Power Definitions and Equations.

As with any other technology, the underlying physics must be understood so that equations and models can be developed that simulate actual behavior.

$i_R(t)$  +  $v_R(t)$  -  
 $\xrightarrow{\hspace{1cm}}$   $i_R(t) = \frac{v_R(t)}{R}$

$$\begin{aligned} i(t) &= I \sin(\omega t), \\ v(t) &= IR \sin(\omega t), \\ \therefore i(t) &\text{ in phase with } v(t) \end{aligned}$$

$\xrightarrow{i_L(t)}$ 
 $+v_L(t)-$ 
 $v_L(t) = L \frac{di(t)}{dt}$

$$\begin{aligned} i(t) &= I \sin(\omega t), \\ v(t) &= \omega L \cos(\omega t), \\ \therefore i(t) &\text{lags } v(t) \text{ by } 90^\circ \end{aligned}$$

$\xrightarrow{i_C(t)}$ 
 $\begin{array}{c} +v_C(t) \\ \text{---} \parallel \text{---} \\ - \end{array}$ 
 $i_C(t) = C \frac{dv(t)}{dt}$

$$\begin{aligned} v(t) &= V \sin(\omega t), \\ i(t) &= \omega C \cos(\omega t), \\ \therefore i(t) &\text{ leads } v(t) \text{ by } 90^\circ \end{aligned}$$

## 1. Power Definitions and Equations, cont.

**Thanks to Charles Steinmetz, Steady-State AC problems are greatly simplified with phasor analysis because differential equations are replaced by complex numbers**

|                  | Time Domain  | Frequency Domain  |
|------------------|--|---|
| <b>Resistor</b>  | $i_R(t) = \frac{v_R(t)}{R}$                                | $Z_R = \frac{\tilde{V}_R}{\tilde{I}_R} = R$                   |
| <b>Inductor</b>  | <p>voltage leads current</p> $v_L(t) = L \frac{di(t)}{dt}$ | $Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} = j\omega L$           |
| <b>Capacitor</b> | <p>current leads voltage</p> $i_C(t) = C \frac{dv(t)}{dt}$ | $Z_C = \frac{\tilde{V}_C}{\tilde{I}_C} = \frac{1}{j\omega C}$ |

## 1. Power Definitions and Equations, cont.

### Voltage and Current Phasors for R's, L's, C's

**Resistor**  $Z_R = \frac{\tilde{V}_R}{\tilde{I}_R} = R, \tilde{V}_R = R\tilde{I}_R$  Voltage and Current in phase  $Q = 0$

---

**Inductor**  $Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} = j\omega L, \tilde{V}_L = j\omega L\tilde{I}_L$  Voltage leads Current by  $90^\circ$   $Q > 0$

---

**Capacitor**  $Z_C = \frac{\tilde{V}_C}{\tilde{I}_C} = \frac{1}{j\omega C}, \tilde{V}_C = \frac{\tilde{I}_C}{j\omega C}$  Current leads Voltage by  $90^\circ$   $Q < 0$

Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015

5

## 1. Power Definitions and Equations, cont.


### Converting Time Domain Waveforms to Phasor Domain

Using a cosine reference,

Voltage cosine has peak = 100V, phase angle =  $-90^\circ$

Current cosine has peak = 50A, phase angle =  $-135^\circ$

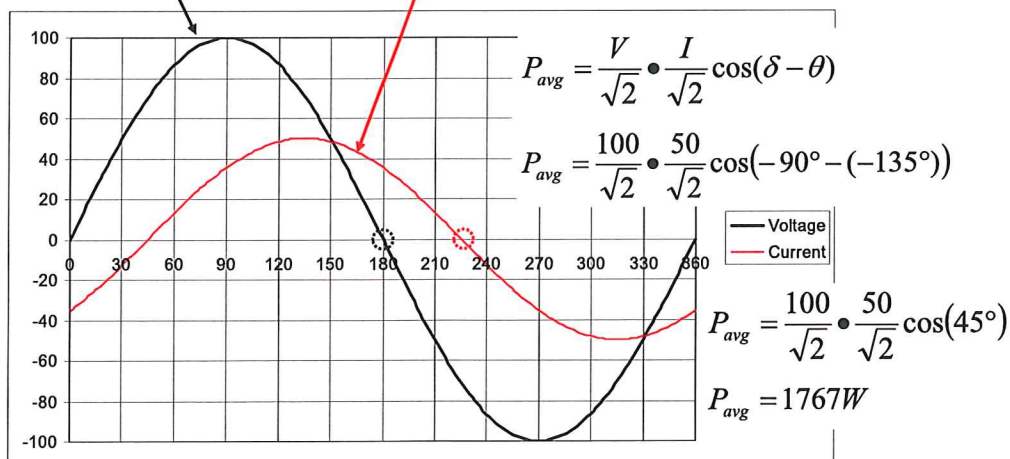Phasors  $\tilde{V} = \frac{100}{\sqrt{2}} \angle -90^\circ V, \tilde{I} = \frac{50}{\sqrt{2}} \angle -135^\circ A$




Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015

6
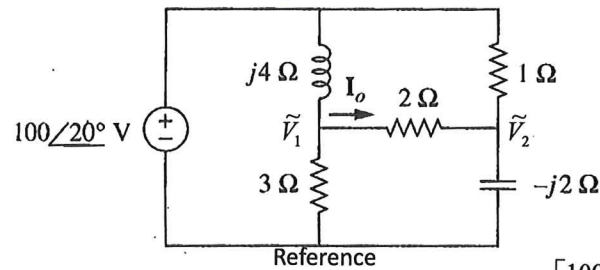
## 1. Power Definitions and Equations, cont.

Circuit analysis using the Nodal Method. Write KCL equations at major nodes 1 and 2, and solve for phasor voltages  $V_1$  and  $V_2$ .



$$\begin{bmatrix} \frac{1}{j4} + \frac{1}{3} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} + 1 + \frac{1}{-j2} \end{bmatrix} \begin{bmatrix} \tilde{V}_1 \\ \tilde{V}_2 \end{bmatrix} = \begin{bmatrix} \frac{100\angle 20^\circ}{j4} \\ \frac{100\angle 20^\circ}{1} \end{bmatrix} \quad \tilde{V}_1 = \frac{\begin{bmatrix} \frac{100\angle 20^\circ}{j4} & -\frac{1}{2} \\ \frac{100\angle 20^\circ}{1} & \frac{1}{2} + 1 + \frac{1}{-j2} \end{bmatrix}}{D}$$

$$D = \left[ \frac{1}{j4} + \frac{1}{3} + \frac{1}{2} \right] \cdot \left[ \frac{1}{2} + 1 + \frac{1}{-j2} \right] - \left[ -\frac{1}{2} \right] \cdot \left[ -\frac{1}{2} \right] \quad \tilde{V}_2 = \frac{\begin{bmatrix} -\frac{1}{2} & \frac{100\angle 20^\circ}{j4} \\ \frac{1}{2} + 1 + \frac{1}{-j2} & \frac{100\angle 20^\circ}{1} \end{bmatrix}}{D}$$

Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015


7

## 1. Power Definitions and Equations, cont.

Active power  $P_{avg}$  and reactive power  $Q$  form a power triangle

$$P_{avg} = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos(\delta - \theta), \quad Q = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \sin(\delta - \theta),$$
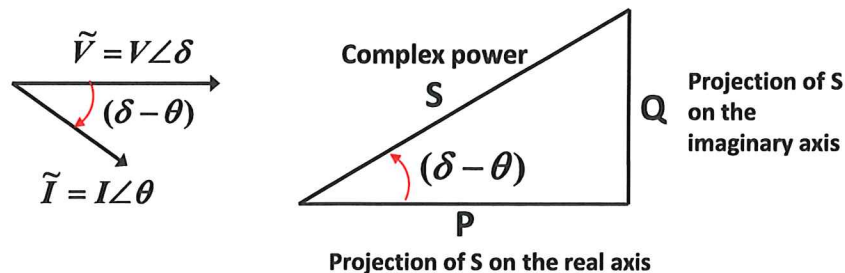
$$S = P + jQ = [\tilde{V}] \cdot [\tilde{I}]^* = [V\angle\delta] \cdot [I\angle\theta]^* = VI\angle(\delta - \theta)$$



$\cos(\delta - \theta)$  is the power factor

Prof. Mack Grady, TAMU Relay Conference  
Tutorial, Topic 1, March 31, 2015

8



## 1. Power Definitions and Equations, cont.

### Resistor

$$S = P + jQ = [\tilde{V}] \cdot \left[ \frac{\tilde{V}}{Z} \right]^* = \frac{V^2}{Z^*} = \frac{V^2}{R}$$

Alternatively,

$$S = P + jQ = [\tilde{I}Z] \cdot [\tilde{I}]^* = I^2 Z = I^2 R$$

Thus  $\Rightarrow P = \frac{V^2}{R} = I^2 R, Q = 0$

### Inductor

$$S = P + jQ = [\tilde{V}] \cdot \left[ \frac{\tilde{V}}{Z} \right]^* = \frac{V^2}{Z^*} = \frac{V^2}{-j\omega L} = j \frac{V^2}{\omega L}$$

Alternatively,

$$S = P + jQ = [\tilde{I}Z] \cdot [\tilde{I}]^* = I^2 Z = j\omega L I^2$$

Thus  $\Rightarrow P = 0, Q = \frac{V^2}{\omega L} = \omega L I^2$   
Inductor consumes reactive power

### Capacitor

$$S = P + jQ = [\tilde{V}] \cdot \left[ \frac{\tilde{V}}{Z} \right]^* = \frac{V^2}{Z^*} = \frac{V^2}{1} = -j\omega C V^2$$

Alternatively,

$$S = P + jQ = [\tilde{I}Z] \cdot [\tilde{I}]^* = I^2 \frac{1}{j\omega C} = -j\omega L I^2$$

Thus  $\Rightarrow P = 0, Q = -\omega C V^2 = \frac{-I^2}{\omega C}$   
Capacitor produces reactive power

**Always use rms values of voltage and current in the above equations**

## 1. Power Definitions and Equations, cont.

**Question:** Why is the sum of power out of a node = 0?

**Answer:** KCL and conservation of power

**Question:** What about reactive power Q?


**Answer:** It depends.

**Question:** Can you be a bit more specific?

**Answer:** Unlike P, there is no physical for Q to be conserved.

When voltage and current are not sinusoidal, then cross products of voltage and current exist and Q is not conserved.

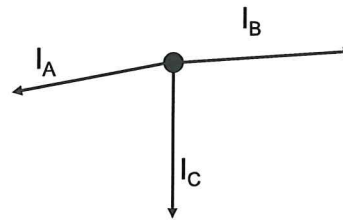But power systems are mostly sinusoidal, so as shown on the right with phasors, both P and Q are conserved.



$$\tilde{I}_A + \tilde{I}_B + \tilde{I}_C = 0$$

$$\tilde{V}(\tilde{I}_A + \tilde{I}_B + \tilde{I}_C) = 0$$

$$\tilde{V}(\tilde{I}_A + \tilde{I}_B + \tilde{I}_C)^* = 0$$

$$P_A + jQ_A + P_B + jQ_B + P_C + jQ_C = 0$$

$$P_A + P_B + P_C = 0$$

$$Q_A + Q_B + Q_C = 0$$