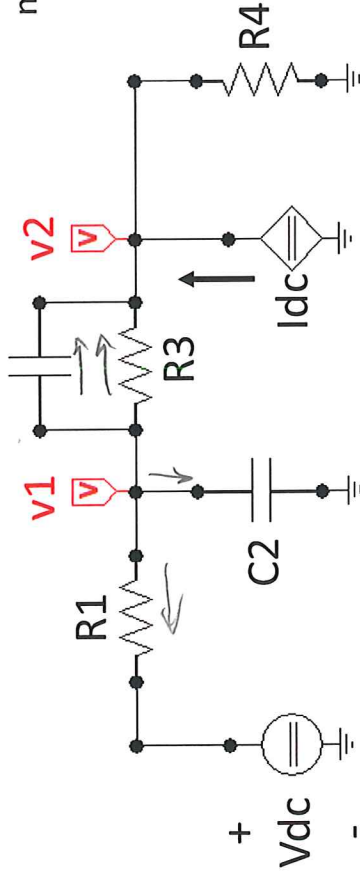


Name: _____

Carefully write the KCL equations for **v1** and **v2** below, and then place them into the organized matrix form on the next page.

$$C1 \quad v_{C1} = (v_1 - v_2)$$



$$v_2 \left[\frac{1}{R_1} + \frac{1}{R_3} \right] + v_2 \left[-\frac{1}{R_3} \right] + \frac{dv_1}{dt} [C_1 + C_2] + \frac{dv_2}{dt} [-C_1] - \frac{V_{dc}}{R_4} = 0$$

$$\frac{v_1 - V_{dc}}{R_1} + C_2 \frac{d}{dt} (v_1 - v_2) + \frac{v_1 - v_2}{R_3} + C_2 \frac{dv_1}{dt} = 0$$

For
Node 1

$$\begin{bmatrix} v_1 \left[-\frac{1}{R_3} \right] \\ v_2 \left[\frac{1}{R_3} + \frac{1}{R_4} \right] \\ \frac{dv_1}{dt} [-C_1] \\ \frac{dv_2}{dt} [C_1] \end{bmatrix}$$

$$\frac{v_2 - v_1}{R_3} + C_1 \frac{d}{dt} (v_2 - v_1) + \frac{v_2}{R_4} - I_{dc} = 0$$

For
Node 2

Name: _____

Initial Conditions & Final Conditions

If $\frac{dv_1}{dt} = 0$, and $\frac{dv_2}{dt} = 0$ $\left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_1 - \frac{1}{R_3}(v_2) = \frac{V_{dc}}{R_1}$
 $-\frac{1}{R_3}v_1 + \left(\frac{1}{R_3} + \frac{1}{R_4}\right)v_2 = I_{dc}$

$\frac{1}{R_1} + \frac{1}{R_2}$	$-\frac{1}{R_3}$	$C_1 + C_2$	$-C_1$	v_1	$=$	$\frac{V_{dc}}{R_1}$
$-\frac{1}{R_3}$	$\frac{1}{R_3} + \frac{1}{R_4}$	$-C_1$	C_1	v_2	$=$	I_{dc}
				dv_1/dt	$=$	
				dv_2/dt	$=$	