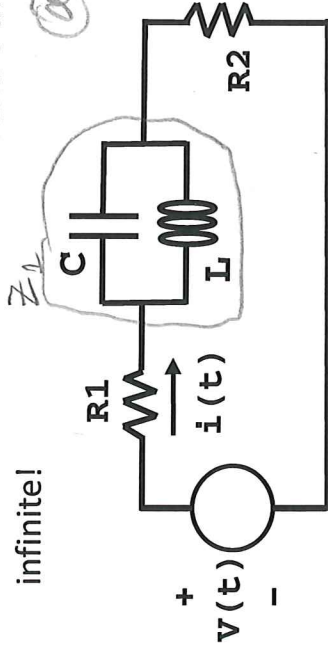


ELC_2323 Test 6, 2021_0423. Make comments. Show your work. Name: _____

Problem 1. The circuit shown below is energized by an AC voltage source $V \cos(\omega t)$.

- Use KVL to develop an equation for phasor current $\tilde{I}$. If you wish, you can define a new variable Z_1 to represent $L \parallel C$. (i.e., L in parallel with C).
- Convert phasor current $\tilde{I}$ to time domain.
- Using the circuit as shown, if C is removed, what will be the new time-domain expression for $i(t)$?
- Determine a combination of L and C that will force $i(t)$ to be zero. Note - neither L or C can be zero or infinite!



$$\textcircled{a} \quad -\tilde{V} + \tilde{I}(R_1 + Z_1 + R_2) = 0$$

$$\tilde{I} = \frac{-\tilde{V}}{R_1 + Z_1 + R_2}, \quad Z_1 = \frac{j\omega L(\frac{1}{j\omega C})}{j\omega L + \frac{1}{j\omega C}} = \frac{L/C}{j[\omega L - \frac{1}{\omega C}]}$$

⑤ Do this by converting $[R_1 + R_2] + Z_1$ to a rectangular form complex number, then to a polar form complex number. Divide polar form $\tilde{V}$ by $\tilde{I}$ to get $\tilde{I}$

③ Z_1 becomes just $j\omega L$.

Repeat the ③, ⑤ processes.

$$\textcircled{d} \quad Z_1 = \frac{L/C}{j[\omega L - \frac{1}{\omega C}]}, \text{ when } \omega L = \frac{1}{\omega C}, \quad \omega L = \frac{1}{\omega C}, \quad \omega^2 LC = 1, \quad LC = \frac{1}{\omega^2}$$


Any combination

ELC_2323 Test 6, 2021_0423. Make comments. Show your work. Name: _____


Ref at peak of voltage waveform

Supply Voltage (Volts)

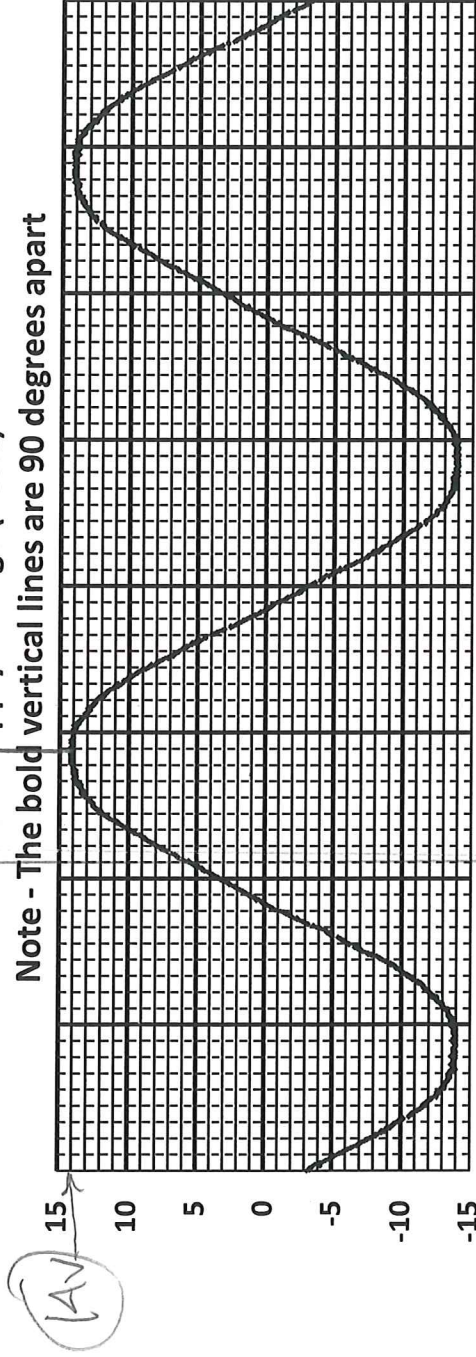Note - The bold vertical lines are 90 degrees apart



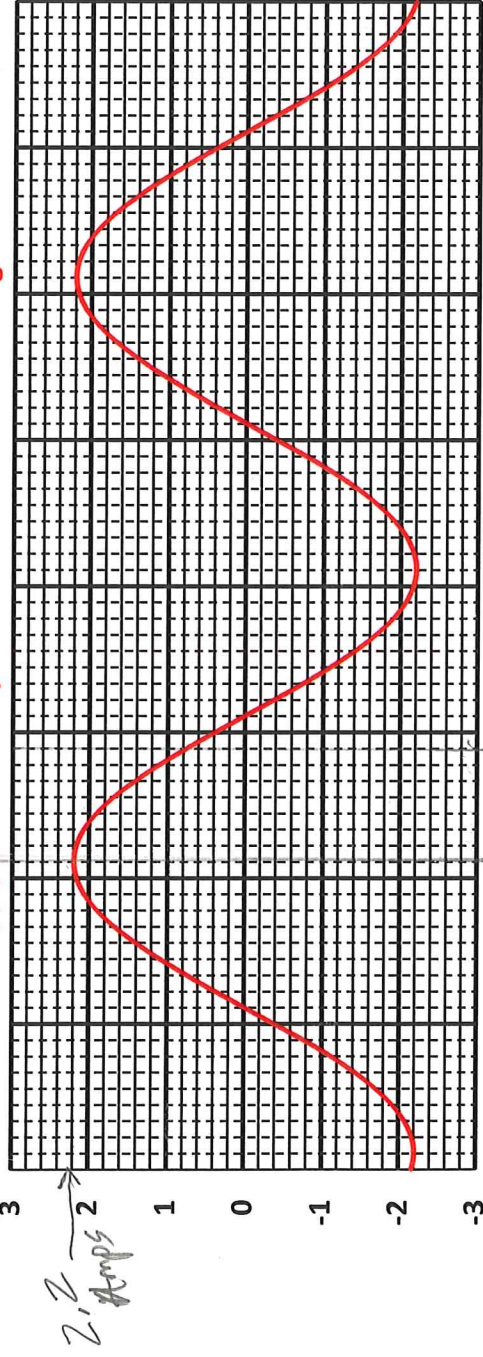Supply Current - Amps. Note - Current Leads Voltage



Current leads by

$\omega = 2\pi f = 2\pi(60) = 120\pi \text{ rad/s}$

Problem 2.

A 60 Hz AC voltage supply (top graph) powers a series combination of capacitor + resistor. No inductor.

- Pick a vertical line for your zero angle reference, and express the two waveforms in time-domain cosine form.
- Convert the time domain waveforms to phasors.
- Compute the combined complex impedance of the capacitor and resistor.
- Compute the capacitor microF and resistor ohms.

$V(t) = 14 \cos(120\pi t) \text{ Volts}$

$i(t) = 2.2 \cos(120\pi t + 70^\circ) \text{ Amps}$

$\tilde{V} = 14 \angle 0$

$\tilde{I} = 2.2 \angle 70^\circ$

$Z = 6.36 \angle -70^\circ = 2.175 - j5.98 \Omega$

$R = 2.175 \Omega$

$\frac{1}{j\omega C} = -j5.98, (j\omega C)(-j5.98) = 1$
 $C = \frac{1}{5.98\omega} = 443 \text{ nF}$