## ECL 4340

## POWER SYSTEMS

LECTURE 11 TRANSMISSION LINE REACTIVE COMPENSATION, Y-BUS MATRIX, POWER FLOWS

> Professor Kwang Y. Lee Department of Electrical and Computer Engineering

1

















**REACTIVE COMPENSATION** 

Reactors are removed during heavy lead: Full load is 1.90 kA at unity pt, 730 kV.

 $= A\left(\frac{130}{\sqrt{3}} \cancel{6}\right) + B\left(1.9 \cancel{6}\right)$ = 442,3 124.8° \$VIA Vs = V3 (442.3) = 766.0 tel

 $V_{RNL} = \frac{V_s}{A} = \frac{766}{0.9313} = 22.6 \quad \text{#}V_{LL}$  $\therefore \quad \text{%} \quad VR = \frac{222.6 - 73\circ}{73\circ} \times 10^{\circ} = 12.68\%$ 

730

a) % Noltage regulation

Vs = A VRFL + B IRFL



8

A=D= cash (XI)= 0.73/3 / <u>a.209</u>° pm B=97.0 / <del>87.2</del>° S-C=1.37 × 10<sup>-3</sup> / <u>90.06</u>° S

 $_{jX'}$   $-j\frac{X'}{2}\left(\frac{N_c}{100}\right)$   $l_B$  $-j\frac{X'}{2}\left(\frac{N_c}{100}\right) = R'$ -16  $\rightarrow$ uu  $-\frac{Y'}{2}\left(\frac{N_L}{100}\right)$  $\frac{1}{2} - \frac{Y'}{2} \left( \frac{N_L}{100} \right) V_{\rm B}$  $\frac{\gamma'}{2}$  $\frac{\gamma'}{2} \neq$ b) Compensation: 75% during light load.  $\frac{Y'}{2} = \frac{Y}{2} \frac{t_{anh}}{Y_{1}} \frac{Y_{e}}{Y_{1}} = (7.011 \times 10^{-4} / \frac{90}{20}) (1.012 / -0.03)$  $= 3.7 \times 10^{-7} + j.7.954 \times 10^{-4} g$ or Y' = 7.4 × 107 + ) 14. 188 × 104 5 With 75% shunt compensation,  $Y_{eg} = 7.4 \times 10^{-7} + 14.188 \times 15^{-4} \left(1 - \frac{75}{106}\right)$ = 3.547 × 10 4 (89.88° S  $\begin{aligned} \mathcal{Z}_{og} &= \mathcal{Z}' = \mathcal{Z} \quad \frac{5\lambda h M}{M} = (97.3 \ \frac{1}{2} \frac{1}{2}$ 







































20



in the system to relate the bus current injections, the bus voltages, and the branch impedances and admittances

## YBUS EXAMPLE Determine the bus admittance matrix for the network shown below, assuming the current injection at each bus *i*

shown below, assuming the <u>current injection</u> at each bus *i* is  $I_i = I_{Gi} - I_{Di}$  where  $I_{Gi}$  is the current injection into the bus from the generator and  $I_{Di}$  is the current flowing into the load





















## Using the $Y_{BUS}$

If the voltages are known then we can solve for the current injections:

 $\mathbf{Y}_{bus}\mathbf{V} = \mathbf{I}$ 

If the current injections are known then we can solve for the voltages:

 $\mathbf{Y}_{bus}^{-1}\mathbf{I} = \mathbf{V} = \mathbf{Z}_{bus}\mathbf{I}$ where  $\mathbf{Z}_{bus}$  is the *bus impedance* matrix

28









