

ECL 4340

POWER SYSTEMS

LECTURE 5

PER-UNIT SYSTEM

Professor Kwang Y. Lee

Department of Electrical and Computer Engineering

Baylor University

1

ANNOUNCEMENT

- Read Chapter 3
- HW 3 is due September 16 in Canvas.

2

3 CALCULATION OF MODEL PARAMETERS

- The parameters of the model are determined based upon
 - nameplate data: gives the rated voltages and power
 - **open circuit test:** rated voltage is applied to primary with secondary open; measure the primary current and losses (the test may also be done applying the voltage to the secondary, calculating the values, then referring the values back to the primary side).
 - **short circuit test:** with secondary shorted, apply voltage to primary to get rated current to flow; measure voltage and losses.

3

4


TRANSFORMER EXAMPLE

Example: A single phase, 100 MVA, 200/80 kV transformer has the following test data:

open circuit: 20 amps, with 10 kW losses

short circuit: 30 kV, with 500 kW losses

Determine the model parameters.

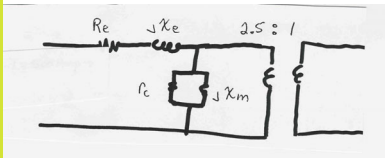

4


5

TRANSFORMER EXAMPLE, CONT'D

A single phase, 100 MVA, 200/80 kV

open circuit: 20 amps, with 10 kW losses

short circuit: 30 kV, with 500 kW losses

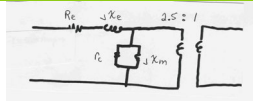

From the short circuit test

$$I_{sc} = \frac{100 \text{ MVA}}{200 \text{ kV}} = 500 \text{ A}, |R_e + jX_e| = \frac{30 \text{ kV}}{500 \text{ A}} = 60 \Omega$$

$$P_{sc} = R_e I_{sc}^2 = 500 \text{ kW} \rightarrow R_e = 2 \Omega,$$

$$\text{Hence } X_e = \sqrt{60^2 - 2^2} = 60 \Omega$$

From the open circuit test

$$R_c = \frac{(200 \text{ kV})^2}{10 \text{ kW}} = 4 \text{ M}\Omega$$


$$|R_e + jX_e + jX_m| = \frac{200 \text{ kV}}{20 \text{ A}} = 10,000 \Omega \quad X_m = 10,000 \Omega$$

5

6

RESIDENTIAL DISTRIBUTION TRANSFORMERS

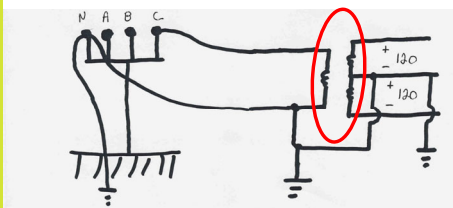Single phase transformers are commonly used in residential distribution systems. Most distribution systems are 4 wire, with a multi-grounded, common neutral.



6

7

VOLTAGE REGULATION

Voltage Regulation:

When the load at the secondary is disconnected suddenly, the voltage at the secondary terminal changes abruptly. The amount of such change (in %) is defined as voltage regulation. Formally, it can be written as

$$\% \text{ regulation} = \frac{|V_{2,NL}| - |V_{2,FL}|}{|V_{2,FL}|} \times 100 \quad (\%)$$

where $V_{2,FL}$: full load (rated) voltage at the secondary
 $V_{2,NL}$: no load (open-circuit) voltage at the secondary.


7

8

VOLTAGE REGULATION

$$\% \text{ regulation} = \frac{|V_{2,NL}| - |V_{2,FL}|}{|V_{2,FL}|} \times 100 \quad (\%)$$

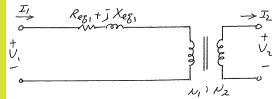where $V_{2,FL}$: full load (rated) voltage at the secondary
 $V_{2,NL}$: no load (open-circuit) voltage at the secondary.



When the secondary is open, $I_2 = 0$. Therefore, $I_1 = 0$. Then, V_1 is applied directly to the N_1 winding of the ideal transformer and V_2 is the voltage induced on the N_2 winding:

$$V_{2,NL} = \left(\frac{N_2}{N_1}\right) V_1$$

8

9

PER-UNIT SYSTEM

Per-Unit System

Power system has many components in a wide range of capacities in different sizes. They also have different voltage ratings. Per-unit system normalizes all variables to values in a manageable level. Moreover, transformers will have the same voltage in per-unit on both windings, thus eliminating the ideal transformers in the circuit diagram.

Per-unit value is defined as

$$pu = \frac{\text{actual value}}{\text{base value}}$$

There are four variables to normalize:

$$V \quad I \quad Z \quad S \quad (P, Q)$$

9

10

PER-UNIT SYSTEM

There are four variables to normalize:

$$V \quad I \quad Z \quad S (P, Q)$$

Normally, base values are selected for V and S and then determine base values for I and Z .

$$I_{base} = \frac{S_{base 1\phi}}{V_{base LN}} = \frac{kVA_{base 1\phi}}{kV_{base LN}}$$

$$Z_{base} = \frac{V_{base LN}}{I_{base}} = \frac{V_{base LN}^2}{S_{base 1\phi}} = \frac{(kV_{base LN})^2 \times 10^3}{kVA_{base 1\phi}} = \frac{(kV_{base LN})^2}{MVA_{base 1\phi}}$$

10

11

PER-UNIT SYSTEM

NOTE: $S = P + jQ$ is normalized by $S_{base 1\phi}$

$$\frac{S}{S_{base 1\phi}} = \frac{P + jQ}{S_{base 1\phi}} = \frac{P}{S_{base 1\phi}} + j \frac{Q}{S_{base 1\phi}}$$

$$\Rightarrow S_{pu} = P_{pu} + j Q_{pu}$$

Thus, we use only one base, $S_{base 1\phi}$, for S , P , and Q .

11

12

PER-UNIT SYSTEM

Per-unit in 3 ϕ system: In 3 ϕ system, we are given $V_{base LL}$ and $S_{base 3\phi}$. By converting these to single phase quantities we have:

$$S_{base 1\phi} = \frac{S_{base 3\phi}}{3}, \quad V_{base LN} = \frac{V_{base LL}}{\sqrt{3}}$$

Then, the base quantities for I and Z are:

$$I_{base} = \frac{S_{base 1\phi}}{V_{base LN}} = \frac{S_{base 3\phi}/3}{V_{base LL}/\sqrt{3}} = \frac{S_{base 3\phi}}{\sqrt{3} V_{base LL}}$$


$$Z_{base} = \frac{V_{base LN}}{I_{base}} = \frac{V_{base LL}/\sqrt{3}}{S_{base 3\phi}/\sqrt{3} V_{base LL}} = \frac{V_{base LL}^2}{S_{base 3\phi}}$$

12

13

PER-UNIT SYSTEM

Example:

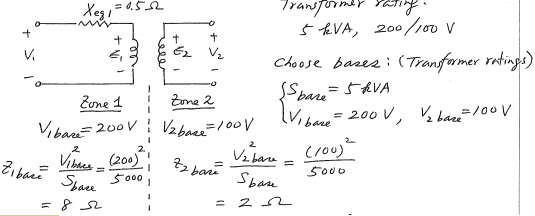

13

14

PER-UNIT SYSTEM

$$Z_{1base} = \frac{V_{1base}^2}{S_{base}} = \frac{(200)^2}{5000} = 8 \text{ } \Omega \quad Z_{2base} = \frac{V_{2base}^2}{S_{base}} = \frac{(100)^2}{5000} = 2 \text{ } \Omega$$

$$X_{eq1} = 0.5 \text{ } \Omega \quad X_{eq2} = \left(\frac{N_2}{N_1}\right)^2 X_{eq1} = \left(\frac{100}{200}\right)^2 (0.5) = 0.125 \text{ } \Omega$$

$$X_{eq1pu} = \frac{0.5}{8} \left(= \frac{X_{eq1}}{Z_{1base}}\right) = 0.0625 \text{ pu} \quad X_{eq2pu} = \frac{0.125}{2} \left(= \frac{X_{eq2}}{Z_{2base}}\right) = 0.0625 = X_{eq1pu}$$

$$E_{1pu} = \frac{E_1}{V_{1base}} = \frac{\left(\frac{N_1}{N_2}\right) E_2}{\left(\frac{N_1}{N_2}\right) V_{2base}} = \frac{E_2}{V_{2base}} = E_{2pu}$$

$$I_{1pu} = \frac{I_1}{I_{1base}} = \frac{\left(\frac{N_2}{N_1}\right) I_2}{\left(\frac{N_2}{N_1}\right) I_{2base}} = \frac{I_2}{I_{2base}} = I_{2pu}$$


14

15

PER-UNIT SYSTEM

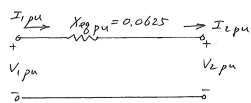Example: Continued

Since $E_{1pu} = E_{2pu}$ and $I_{1pu} = I_{2pu}$, and $X_{1pu} = X_{2pu}$, we have the following equivalent circuit:



15

16

PER UNIT CALCULATIONS

- A key problem in analyzing power systems is the large number of transformers.
 - It would be very difficult to continually have to refer impedances to the different sides of the transformers
- This problem is avoided by a normalization of all variables.
- This normalization is known as per unit analysis.

$$\text{quantity in per unit} = \frac{\text{actual quantity}}{\text{base value of quantity}}$$

16

17

PER UNIT CONVERSION PROCEDURE, 1 Φ

1. Pick a 1 ϕ VA base for the entire system, S_B
2. Pick a voltage base for each different voltage level, V_B . Voltage bases are related by transformer turns ratios. Voltages are line to neutral.
3. Calculate the impedance base, $Z_B = (V_B)^2/S_B$
4. Calculate the current base, $I_B = V_B/Z_B$
5. Convert actual values to per unit

Note, per unit conversion affects magnitudes, not the angles. Also, per unit quantities no longer have units (i.e., a voltage is 1.0 p.u., **not** 1 p.u. volts)

17

18

PER UNIT SOLUTION PROCEDURE


1. Convert to per unit (p.u.) (many problems are already in per unit)
2. Solve
3. Convert back to actual as necessary

18

19

PER UNIT EXAMPLE

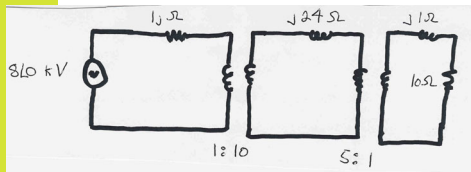Solve for the current, load voltage and load power in the circuit shown below using per unit analysis with an S_B of 100 MVA, and voltage bases of 8 kV, 80 kV and 16 kV.




Original Circuit


19

20

PER UNIT EXAMPLE, CONT'D

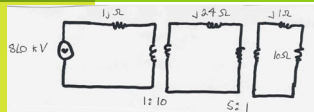

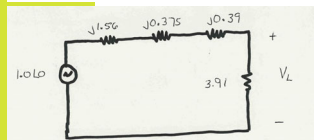with an S_B of 100 MVA, and voltage bases of 8 kV, 80 kV and 16 kV.



Same circuit, with values expressed in per unit.

$$Z_B^{Left} = \frac{8kV^2}{100MVA} = 0.64\Omega$$

$$Z_B^{Middle} = \frac{80kV^2}{100MVA} = 64\Omega$$

$$Z_B^{Right} = \frac{16kV^2}{100MVA} = 2.56\Omega$$

$$Z^{Left} = \frac{1\Omega}{0.64\Omega} = 1.56p.u.$$


$$Z^{Middle} = \frac{24\Omega}{64\Omega} = 0.375p.u.$$

$$Z^{Right} = \frac{1\Omega}{2.56\Omega} = 0.39p.u.$$

20

21

PER UNIT EXAMPLE, CONT'D

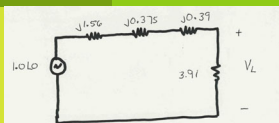

$$I = \frac{1.0\angle 0^\circ}{3.91 + j2.327} = 0.22\angle -30.8^\circ \text{ p.u. (not amps)}$$

$$V_L = 1.0\angle 0^\circ - 0.22\angle -30.8^\circ \times 2.327\angle 90^\circ$$

$$= 0.859\angle -30.8^\circ \text{ p.u.}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

$$S_G = 1.0\angle 0^\circ \times 0.22\angle 30.8^\circ = 0.22\angle 30.8^\circ \text{ p.u.}$$

21

22

PER UNIT EXAMPLE, CONT'D

To convert back to actual values just multiply the per unit values by their per unit base

$$V_L^{\text{Actual}} = 0.859 \angle -30.8^\circ \times 16 \text{ kV} = 13.7 \angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189 \angle 0^\circ \times 100 \text{ MVA} = 18.9 \angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22 \angle 30.8^\circ \times 100 \text{ MVA} = 22.0 \angle 30.8^\circ \text{ MVA}$$

$$I_B^{\text{Middle}} = \frac{100 \text{ MVA}}{80 \text{ kV}} = 1250 \text{ Amps}$$

$$I_{\text{Middle}}^{\text{Actual}} = 0.22 \angle -30.8^\circ \times 1250 \text{ Amps} = 275 \angle -30.8^\circ \text{ A}$$

22

THREE PHASE PER UNIT

Procedure is very similar to 1 ϕ except we use a 3 ϕ VA base, and use line to line voltage bases

1. Pick a **3 ϕ** VA base for the entire system, $S_B^{3\phi}$
2. Pick a voltage base for each different voltage level, V_B . **Voltages are line to line.**
3. Calculate the impedance base

$$Z_B = \frac{V_{B,LL}^2}{S_B^{3\phi}} = \frac{(\sqrt{3} V_{B,LN})^2}{3 S_B^{1\phi}} = \frac{V_{B,LN}^2}{S_B^{1\phi}}$$

Exactly the same impedance bases as with single phase!

23

23

THREE PHASE PER UNIT, CONT'D

4. Calculate the current base, I_B

$$I_B^{3\phi} = \frac{S_B^{3\phi}}{\sqrt{3} V_{B,LL}} = \frac{3 S_B^{1\phi}}{\sqrt{3} \sqrt{3} V_{B,LN}} = \frac{S_B^{1\phi}}{V_{B,LN}} = I_B^{1\phi}$$

Exactly the same current bases as with single phase!


5. Convert actual values to per unit

24

24

THREE PHASE PER UNIT EXAMPLE

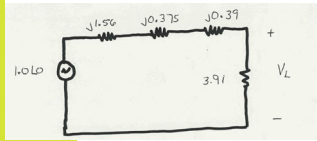Solve for the current, load voltage and load power in the previous circuit, assuming a 3 ϕ power base of **300 MVA**, and line to line voltage bases of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 ϕ example voltages). Also assume the generator is Y-connected so its line to line voltage is 13.8 kV.



Convert to per unit as before. Note the system is exactly the same!

25

25

3 ϕ PER UNIT EXAMPLE, CONT'D

$$I = \frac{1.0\angle 0^\circ}{3.91 + j2.327} = 0.22\angle -30.8^\circ \text{ p.u. (not amps)}$$

$$V_L = 1.0\angle 0^\circ - 0.22\angle -30.8^\circ \times 2.327\angle 90^\circ \\ = 0.859\angle -30.8^\circ \text{ p.u.}$$

$$S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189 \text{ p.u.}$$

$$S_G = 1.0\angle 0^\circ \times 0.22\angle 30.8^\circ = 0.22\angle 30.8^\circ \text{ p.u.}$$

Again, analysis is exactly the same!

26

26

3 ϕ PER UNIT EXAMPLE, CONT'D

Differences appear when we convert back to actual values

$$V_L^{\text{Actual}} = 0.859\angle -30.8^\circ \times 27.6 \text{ kV} = 23.8\angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189\angle 0^\circ \times 300 \text{ MVA} = 56.7\angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22\angle 30.8^\circ \times 300 \text{ MVA} = 66.0\angle 30.8^\circ \text{ MVA}$$

$$I_B^{\text{Middle}} = \frac{300 \text{ MVA}}{\sqrt{3} \times 138 \text{ kV}} = 1250 \text{ Amps (same current!)}$$


$$I_{\text{Middle}}^{\text{Actual}} = 0.22\angle -30.8^\circ \times 1250 \text{ Amps} = 275\angle -30.8^\circ \text{ A}$$

27

27

3Φ PER UNIT EXAMPLE 2

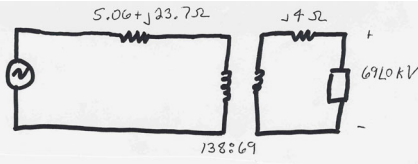Assume a 3Φ load of $100+j50$ MVA with V_{LL} of 69 kV is connected to a source through the below network:



What is the supply current and complex power?

Answer: $I=467$ amps, $S = 103.3 + j76.0$ MVA

28

28

PER-UNIT CHANGE ON NEW BASE

29

Changing Per-Unit Values to Different Bases:

Normally, the per-unit (or percent) impedances of equipment are specified on the equipment base, which generally will be different from the power system base.

Since all impedances in the system must be expressed on the same base for per-unit (or percent) calculations, it is necessary to convert all values to the "common base" selected.

29

PER-UNIT SYSTEM

30

Recall the definition of the per-unit:

$$pu = \frac{\text{actual}}{\text{base old}} \quad pu = \frac{\text{actual}}{\text{base new}}$$

By dividing the two equations:

$$\frac{pu_{\text{new}}}{pu_{\text{old}}} = \frac{\text{base old}}{\text{base new}} \quad \text{or} \quad pu_{\text{new}} = pu_{\text{old}} \left(\frac{\text{base old}}{\text{base new}} \right)$$

Applying this to per-unit impedance,

$$z_{pu \text{ new}} = z_{pu \text{ old}} \frac{z_{\text{base old}}}{z_{\text{base new}}} = z_{pu \text{ old}} \frac{\frac{V_{\text{base old}}^2}{S_{\text{base old}}}}{\frac{V_{\text{base new}}^2}{S_{\text{base new}}}}$$

$$\therefore z_{pu \text{ new}} = z_{pu \text{ old}} \left(\frac{V_{\text{base old}}}{V_{\text{base new}}} \right)^2 \left(\frac{S_{\text{base new}}}{S_{\text{base old}}} \right)$$

30

31

TRANSFORMER REACTANCE

- Transformer reactance is often specified as a percentage, say 10%. This is a per unit value (multiplied by 100) on the power base of the transformer.
- ❖ Example: A 54 MVA transformer has a leakage reactance of 3.69%. What is the reactance on a 100 MVA base?

$$X_e = 0.0369 \times \frac{100}{54} = 0.0683 \text{ p.u.}$$

31

32

TRANSFORMER REACTANCE

- Example: A 350 MVA, 230/20 kV transformer has leakage reactance of 10%. What is p.u. value on 100 MVA base? What is value in ohms (230 kV)?

$$X_e = 0.10 \times \frac{100}{350} = 0.0286 \text{ p.u.}$$


$$0.0286 \times \frac{230^2}{100} = 15.1 \Omega$$

32

33

PER-UNIT SYSTEM

Example:

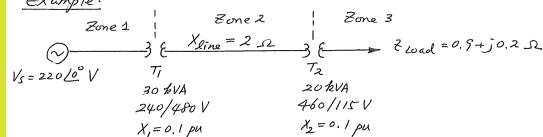

The system is 1 φ. Use base values of T_1 for the entire system. Draw the per-unit impedance diagram and find the load current.


$S_{base} = 30 \text{ MVA}$ (T_1) for the whole system, System Base.

33

34

PER-UNIT SYSTEM

Example:

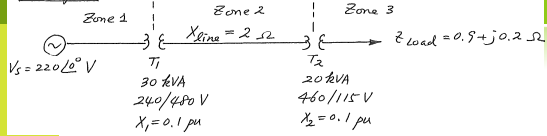


$S_{base} = 30 \text{ kVA}$ (T_1) for the whole system, System Base.

However, there are three different base voltages, one for each zone: Again using the voltages of T_1 ,

V_{base}	$V_{base1} = 240 \text{ V}$	$V_{base2} = 480 \text{ V}$	$V_{base3} = 480 \left(\frac{115}{480} \right) = 120 \text{ V}$
Z_{base}	$Z_{base1} = \frac{(240)^2}{30,000} = 1.92 \Omega$	$Z_{base2} = \frac{(480)^2}{30,000} = 7.68 \Omega$	$Z_{base3} = \frac{(120)^2}{30,000} = 0.48 \Omega$
I_{base}			$I_{base3} = \frac{30,000}{120} = 250 \text{ A}$

34

Example:

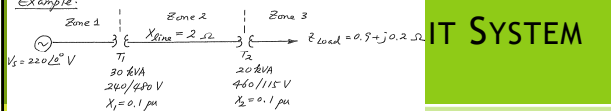

IT SYSTEM

Next, convert the per-unit impedance of T_2 using the system base values:

$$X_2 = (0.1) \left(\frac{480}{120} \right)^2 \left(\frac{30,000}{20,000} \right) = 0.1378 \text{ pu}$$

$$\text{or } X_2 = (0.1) \left(\frac{115}{120} \right)^2 \left(\frac{30,000}{20,000} \right) = 0.1378 \text{ pu}$$

The line, located in Zone 2, has the per-unit impedance

$$X_{line \text{ pu}} = \frac{X_{line}}{Z_{base2}} = \frac{2}{7.68} = 0.2604 \text{ pu}$$

The load, located in Zone 3, has the per-unit impedance

$$Z_{load \text{ pu}} = \frac{Z_{load}}{Z_{base3}} = \frac{0.9 + j0.2}{0.48} = 1.875 + j0.416 \text{ pu}$$

The source, located in Zone 1, has the per-unit voltage


$$V_s \text{ pu} = \frac{V_s}{V_{base1}} = \frac{220 \angle 0^\circ}{240} = 0.9167 \angle 0^\circ \text{ pu}$$

35

36

PER-UNIT SYSTEM

The per-unit impedance diagram is now,

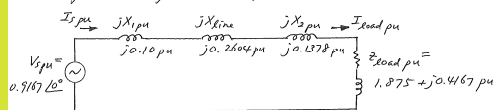

The load current is then

$$\begin{aligned} I_{load \text{ pu}} &= I_s \text{ pu} = \frac{V_s \text{ pu}}{j(X_1 \text{ pu} + X_{line \text{ pu}} + X_2 \text{ pu}) + Z_{load \text{ pu}}} \\ &= \frac{0.9167 \angle 0^\circ}{j(0.10 + 0.2604 + 0.1378) + (1.875 + j0.4167)} \\ &= \frac{0.9167 \angle 0^\circ}{1.875 + j0.9149} = \frac{0.9167 \angle 0^\circ}{2.086 \angle 26.01^\circ} = 0.4395 \angle -26.01^\circ \text{ pu} \end{aligned}$$

36

37

PER-UNIT SYSTEM

The actual load current is

$$I_{\text{load}} = (Z_{\text{load pu}}) I_{\text{base3}} = (0.4335 \angle -26.01^\circ) (250 \text{ A})$$

$$= \underline{\underline{108.8 \angle -26.01^\circ \text{ A}}}$$

Question: How can you find the current from the source?
 How about the current in the line?
 How can you find the voltage at the load?

37